

IEET 231 Lecture 25 Motor Starters/Controls


- ! There are about 1 Billion motors in service in the United States
 - ! Motors account for 67% of the total U.S. electric energy use
 - ! Only 2% of motors are bigger than 5 hp
 - ! That 2% accounts for 70% of the energy used by motors
- From the Electric Power Research Institute (EPRI)

OBJECTIVES


- Draw a schematic for a basic motor starter, including push button controls and overload protection.
- Know the symbols for and the principles of operation for normally open and closed relays (with or without time delay), push buttons, and coils.

Slide 1 of 17

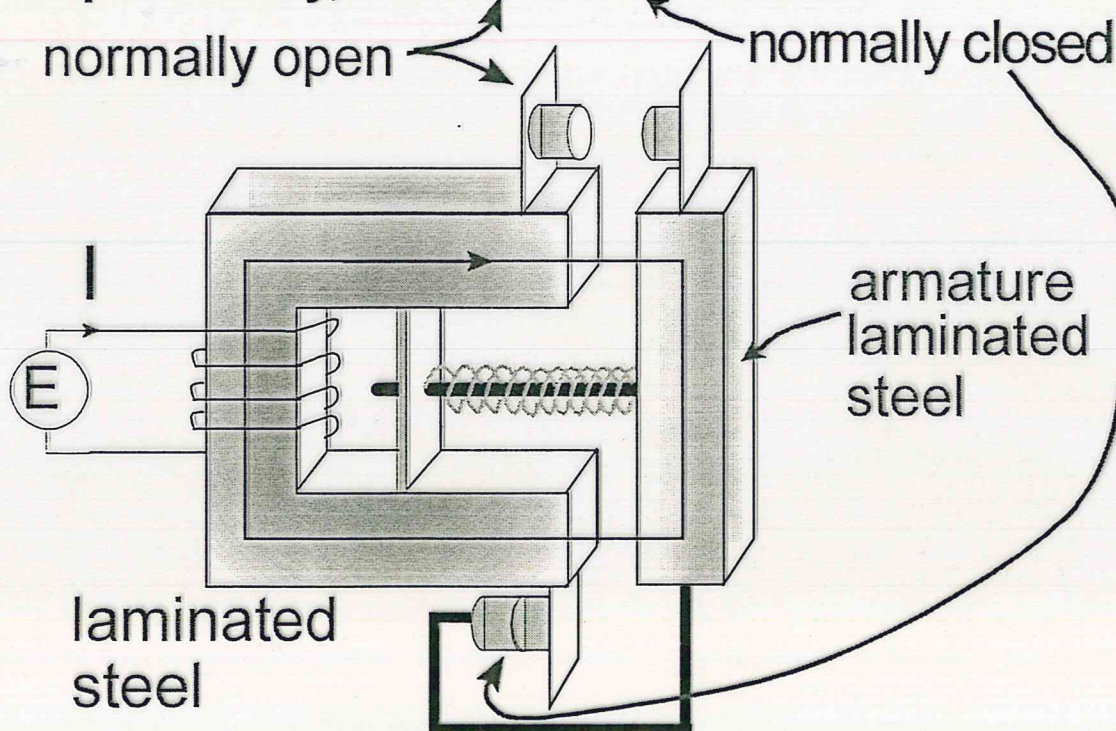Simplified relay, with NO and NC contacts




Slide 2 of 17

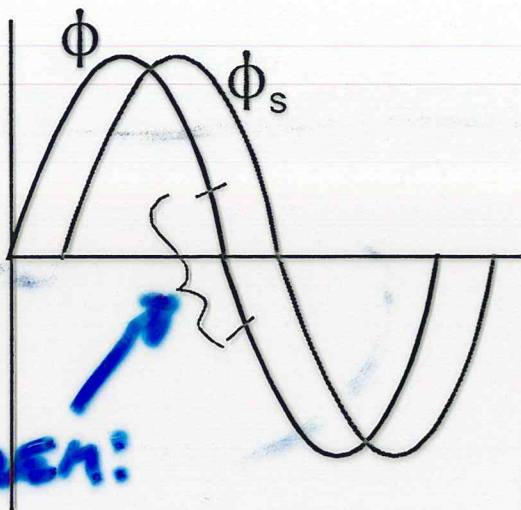

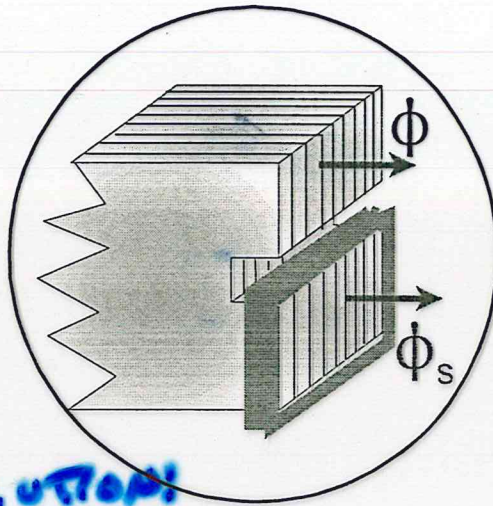PROBLEM!

relay unlatches when flux goes through zero then pulls in again \rightarrow chatter



SOLUTION!

shading pole causes a flux component out of phase with orig. flux \rightarrow no chatter

Slide 3 of 17

Symbols

General contacts




N.O.

normal means the power off or deenergized state




N.C.

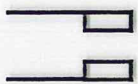


pow. off



pow. on

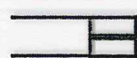


pow. off

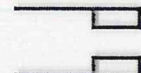


pow. on


Pushbutton contacts (PB)

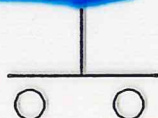

NO - push to start

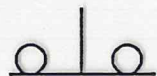

NC - push to stop

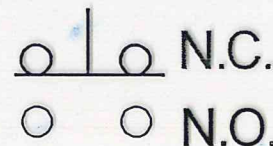



dual contacts single PB

Slide 4 of 17



Time delay contacts

1. delay on energization

n.o., time to close

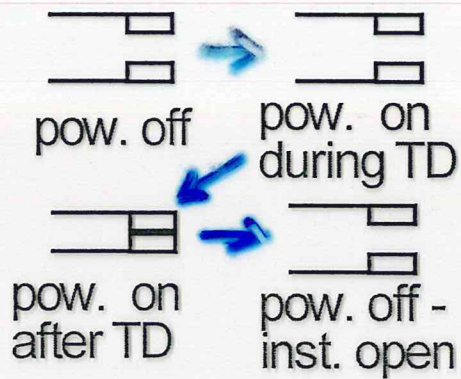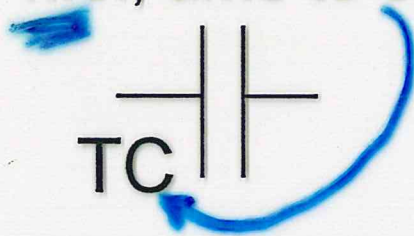


n.c., time to open

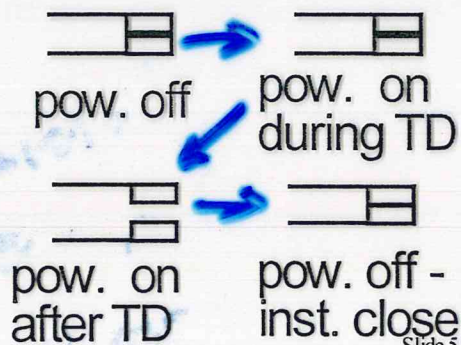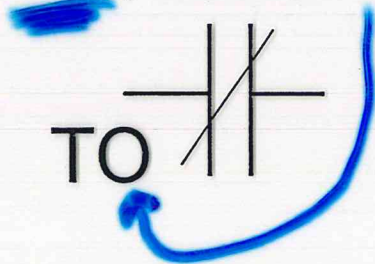



Slide 5 of 17

2. delay on de-energization


n.o., time to open

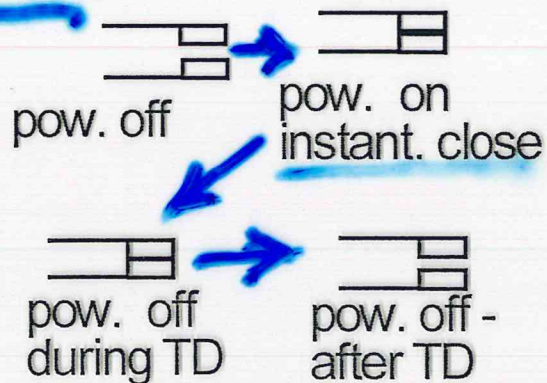

n.c., time to close

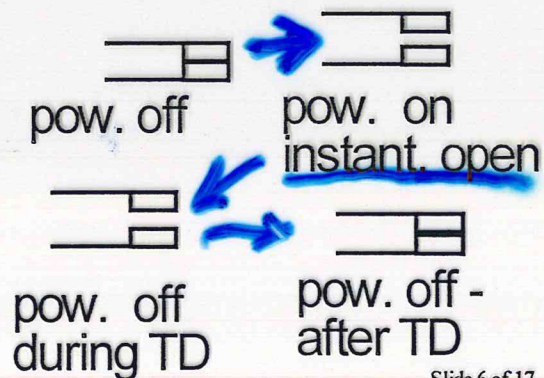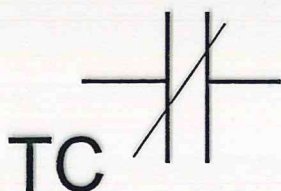

Slide 6 of 17

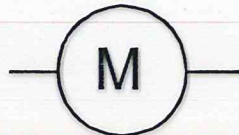


Magnet coil

C - contactor

M - motor starter

H - heater


X - auxiliary

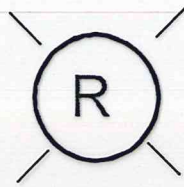


Lamp

G

B

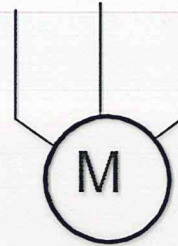

Motor

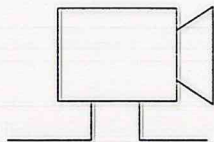


Horn

*INCOMING
POWER FOR
3 PHASES*

Slide 7 of 17

Motor Starters

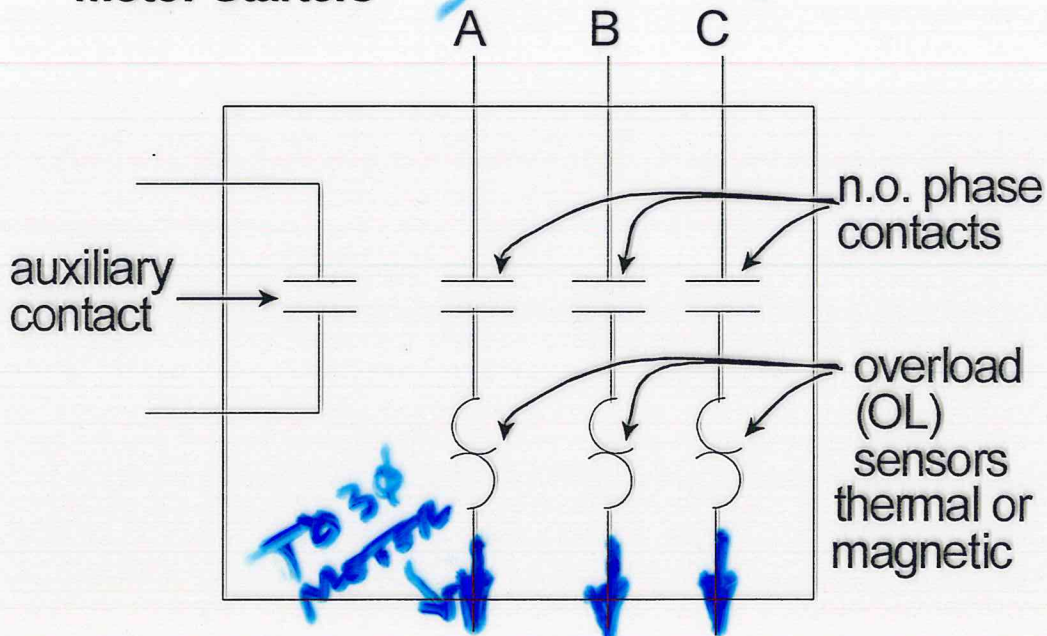

OL sensors detect abnormal conditions (overload or single phasing) and provide signal to shut down if necessary

Slide 8 of 17

Bimetallic overload


cold



hot



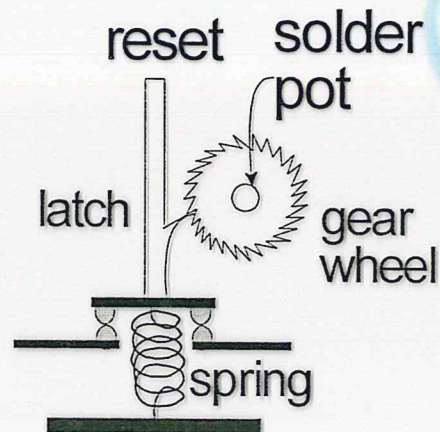different metals expand at diff. rates when heated so contact bends away when too hot



Melting alloy overload

(THIS MELTS)

Slide 9 of 17

Types of overload detectors

Thermal can be affected by ambient temp. & are thus less precise, but can be mounted in windings for very accurate indication of overheating

Magnetic detect B field due to currents in winding. Very good for detecting single phasing

Electronic obtain signal from sensor and cause relay to operate

Slide 10 of 17

Motor starters and contactors can control large amounts of power with low-voltage, low power devices

Thus, there are two circuits involved:


- power circuit
- control circuit

each of which is wired independently


However, their operations are interdependent

Slide 11 of 17

Wiring a motor starter

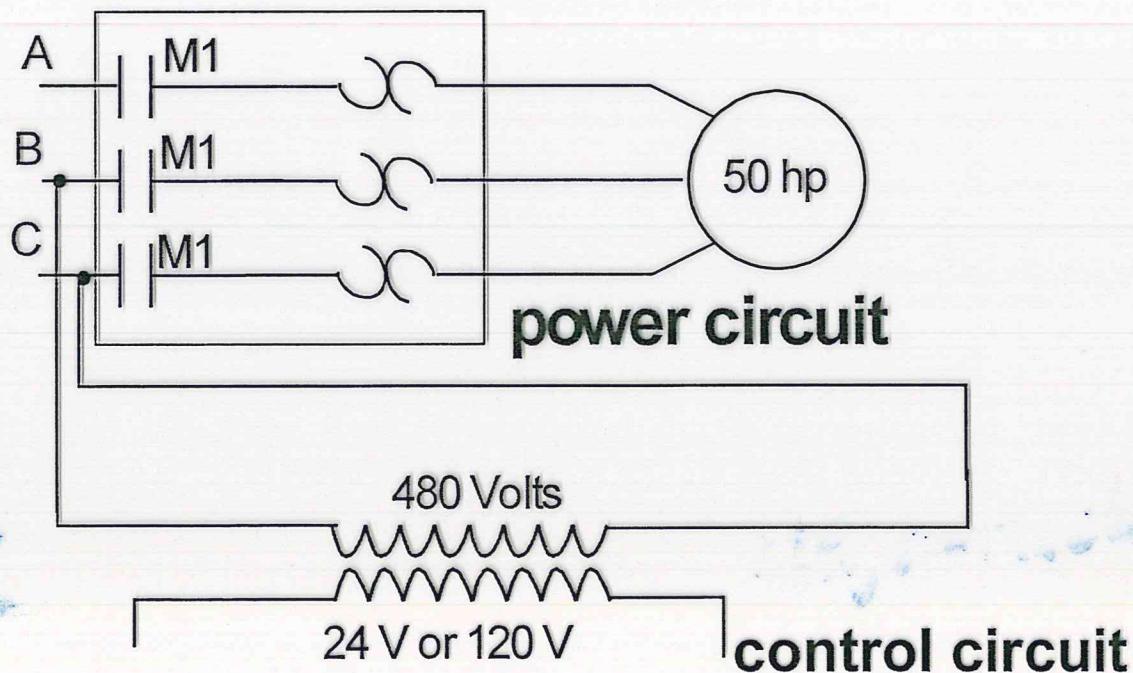

Slide 12 of 17

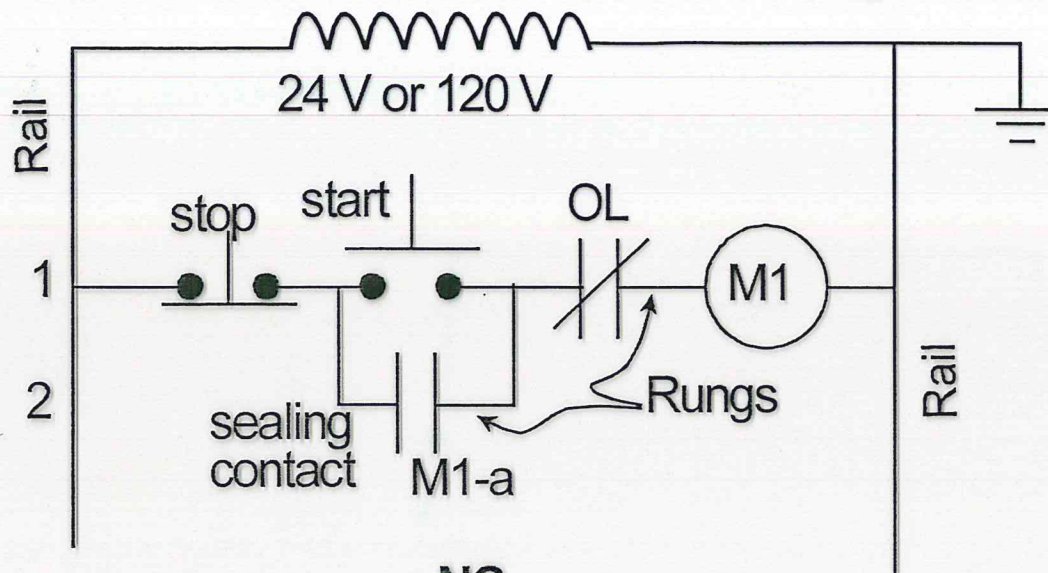


OL relay is drawn as a **NC** relay, but only opens when there is an overload

Sealing (or holding) relay keeps ckt on when start is released

Sides are rails, cross-paths are rungs → **ladder diagram**

Slide 13 of 17

Two and three wire control

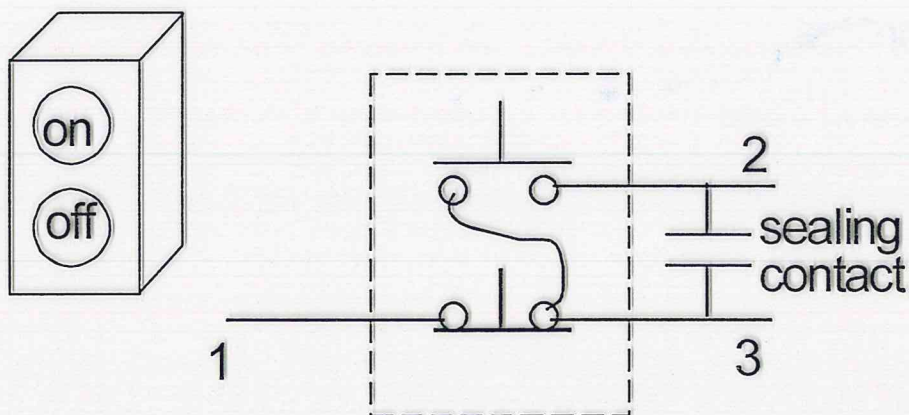

3 wire control ≡ undervoltage control

(i.e., voltage ↓ relay unlatches)

If relay unlatches, system must be restarted


Slide 14 of 17

2 wire control:


undervoltage release

if voltage drops, coil
can't hold relay
closed and system
shuts down

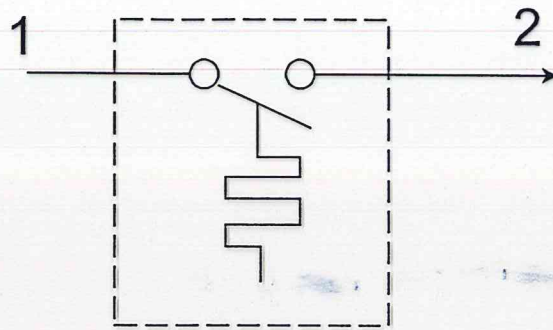returns to service
whenever voltage is
restored




thermostat

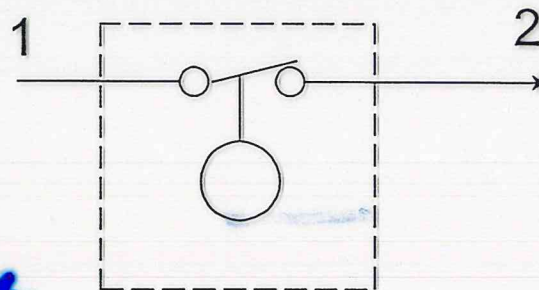

float switch

Slide 15 of 17


EXAMPLE
3-WIRE
control

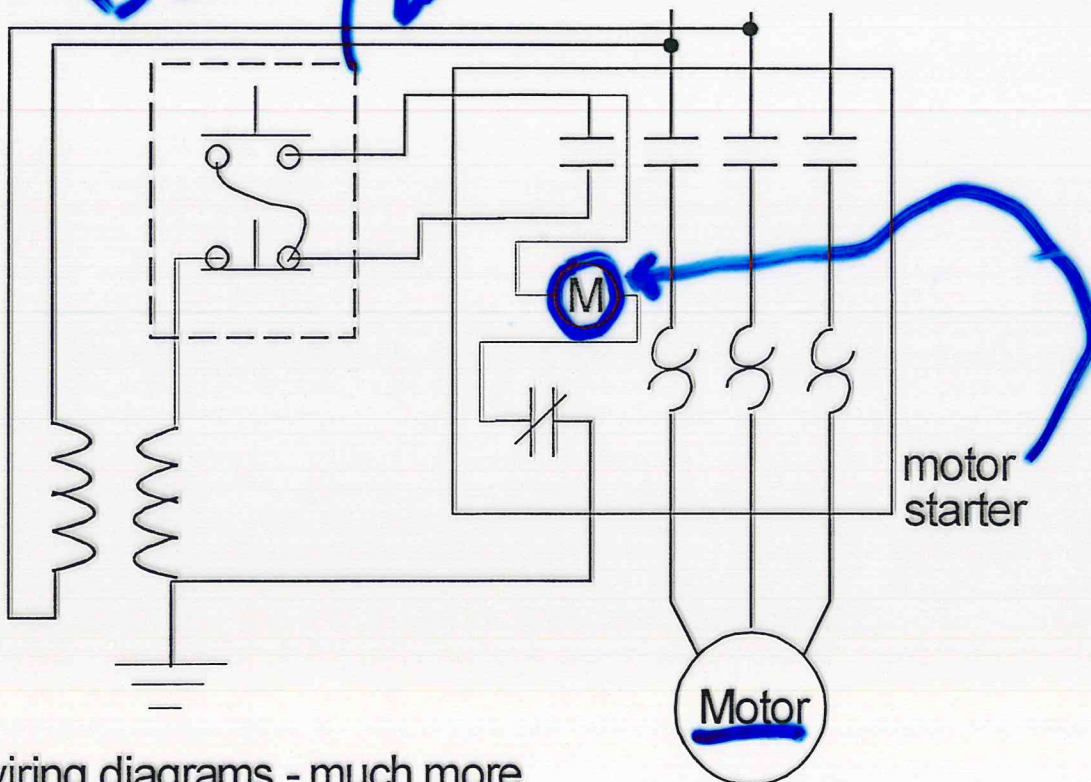

wiring diagrams - much more
difficult to work from

Slide 16 of 17

EXAMPLE
2-WIRE SYSTEM

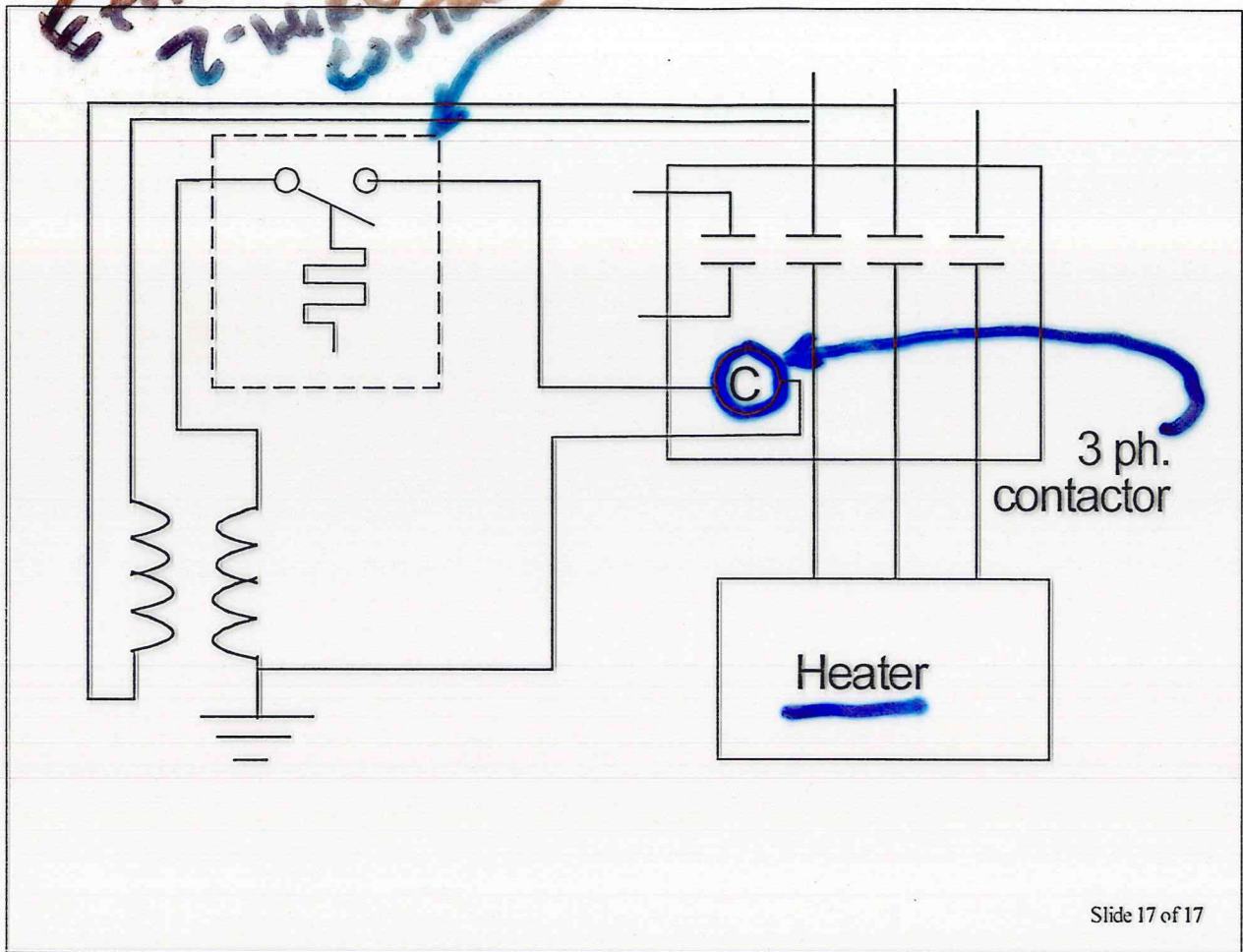

EET 231 Lecture 26

Ladder diagram development

Objectives:

- a. Be able to construct a ladder diagram for a control circuit given the operational requirements for the system.
- b. Given a ladder diagram:

Identify the purpose of each component
Identify what each component is
Properly label the rung numbers to the left of left rail
Properly label control functions to the right of the right rail
Describe the operation of the control circuit

Slide 1 of 17

Steps for developing a ladder diagram

Process is as much an art as science, however, certain steps can be followed:

1. Consider system, make sketch of all components
2. List out the desired operating sequence - table, sentences, or state-diagram
3. Draw ladder diagram to achieve desired operation
4. Verify operation of ladder diagram
manually run through operation
list each device when operated
cross off each device when deactivated
End of cycle → **everything should be crossed off**

Slide 2 of 17


Some similarities to digital circuit design

- AND function

two or more things must happen

"A and B"

TO ENERGIZE THIS
RELAY (COIL)

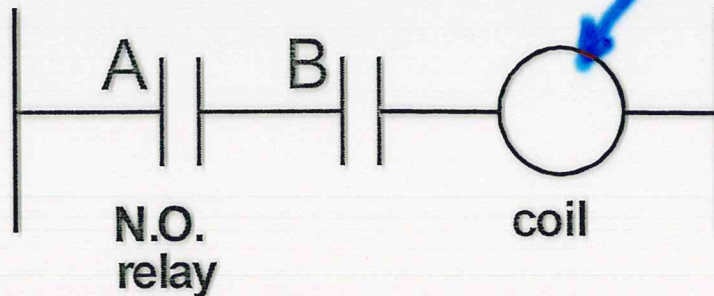


Slide 3 of 17

- OR function


one or both things must happen

"A or B"

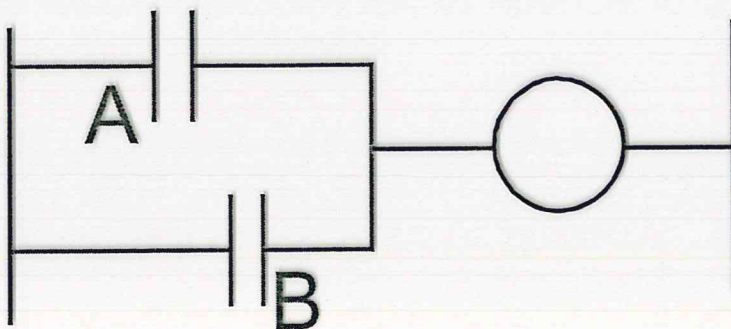

Slide 4 of 17

- NOT

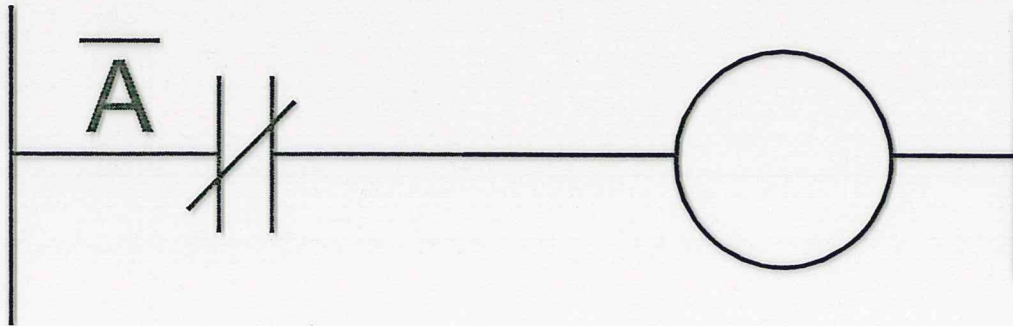


Slide 5 of 17

- XOR (exclusive or)

(\overline{A} and B) or (A and \overline{B})


BOOLEAN
ALGEBRA

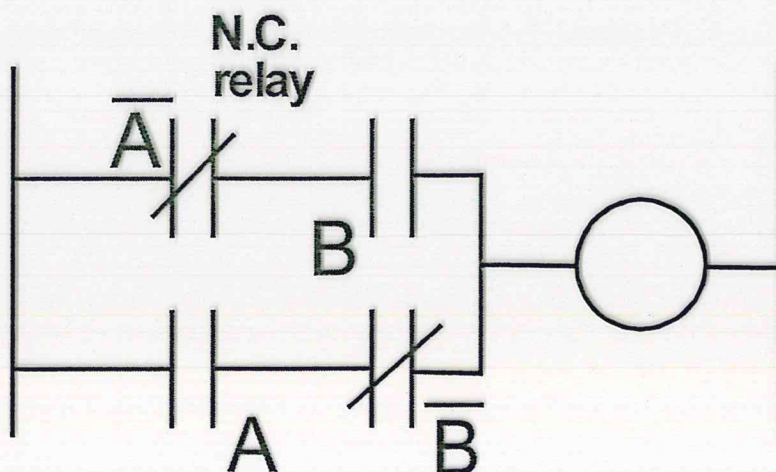

Slide 6 of 17

Conventions for ladder diagrams

- power source may not be shown

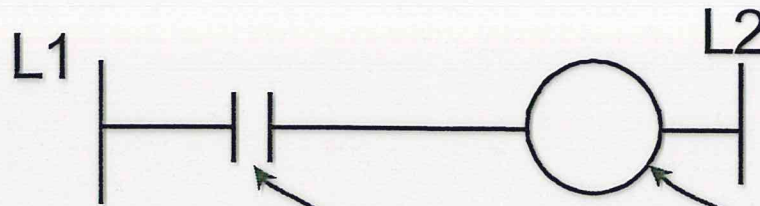

- switches and relays are inputs and go on the left side of the rungs


- lamps, coils, horns, etc are outputs and go on the right side of the rungs

Slide 7 of 17

Conventions for ladder diagrams

- all OL relays may be shown as one

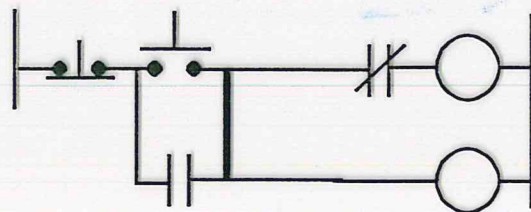- one input can control multiple outputs in parallel



- rungs are consecutively numbered from top to bottom to the left of the left rung

Slide 8 of 17

Conventions for ladder diagrams

- rungs are consecutively numbered from top to bottom to the left of the left rung
- sequence of operation is generally from top to bottom but some skipping around may occur
- any given relay, contactor, or motor starter may have multiple contacts which can be used anywhere in the diagram
- rung numbers of controlled contacts are placed to the right of the right rung. Underlined numbers indicate a normally closed contact
- contacts are labeled with the same alphanumeric designation as the coil that controls them

Slide 9 of 17

Example

Design controls for a heater and blower device

Specifications:

- circuit should have manual on-off control
 - ∴ requires a start/stop pushbutton set
- blower shouldn't come on until heater is warm
- ∴ need thermostat or time delay relay

Slide 10 of 17


Example

(CONT)

Specifications:


- green light on whenever start switch is on to the control circuit and heater is off

\bar{B}

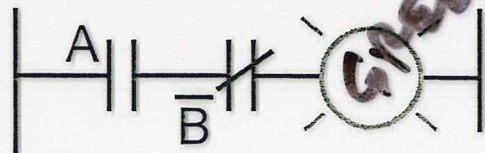

- red light when the heater is on

B

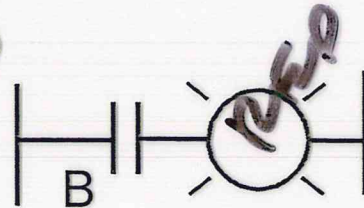

Slide 11 of 17

Example

(CONT)

Specifications:


- heater/blower turns off when desired temperature is reached

∴ need thermostat

- once turned on, device should cycle on and off as temperature changes

∴ control power stays on when thermostat shuts off heater and blower

Slide 12 of 17

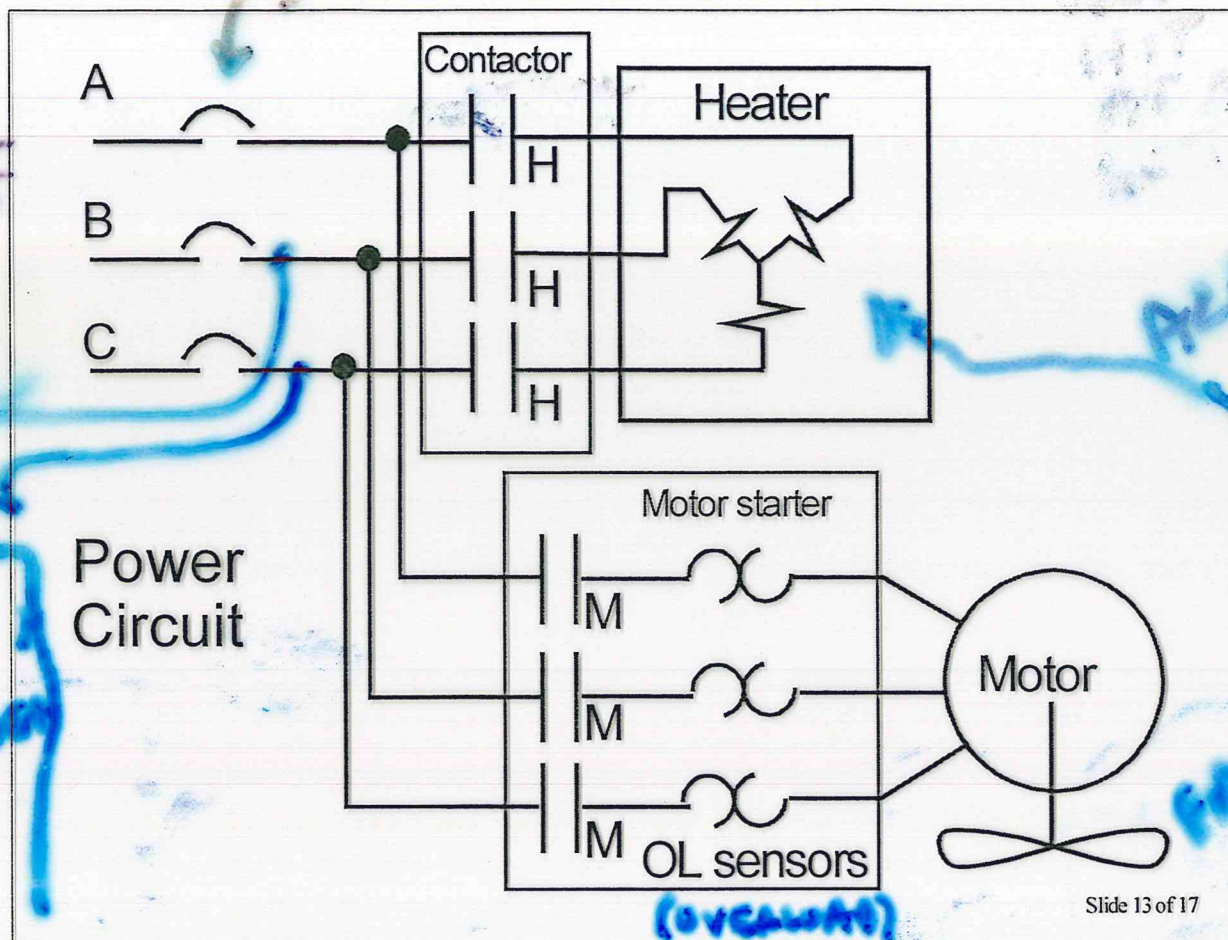

State


State Condition

- | | |
|---|---|
| 0 | No power available, system is dead |
| 1 | System is completely off, left rail of ladder diagram is hot (CONTROL POWER ON) |
| 2 | Control power on, thermostat off, green on |
| 3 | Thermostat closed, heater on, green off, red on (i.e., WE WANT HEAT) |
| 4 | Same as 3, but motor is on |
| 5 | Everything shut down due to motor OL OL tripped |


NOTE:

1. from any state a power failure goes back to st. zero
2. from any state > 1, push stop to return to state 1
3. from state 5, reset OL to return to state 1

Create State Diagram:

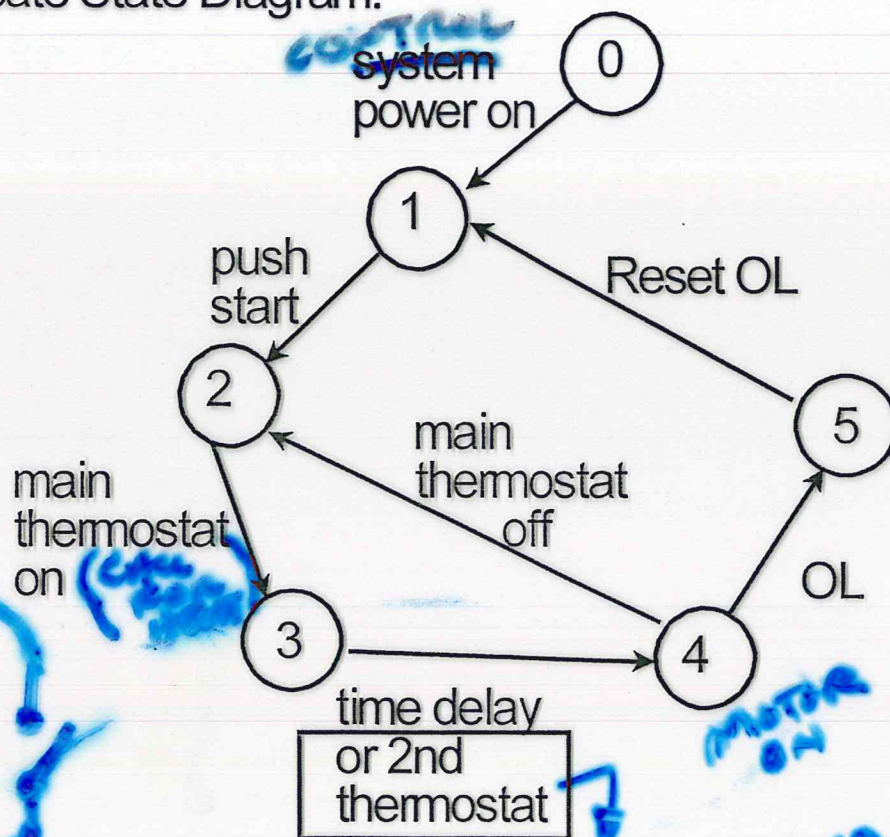


Slide 15 of 17

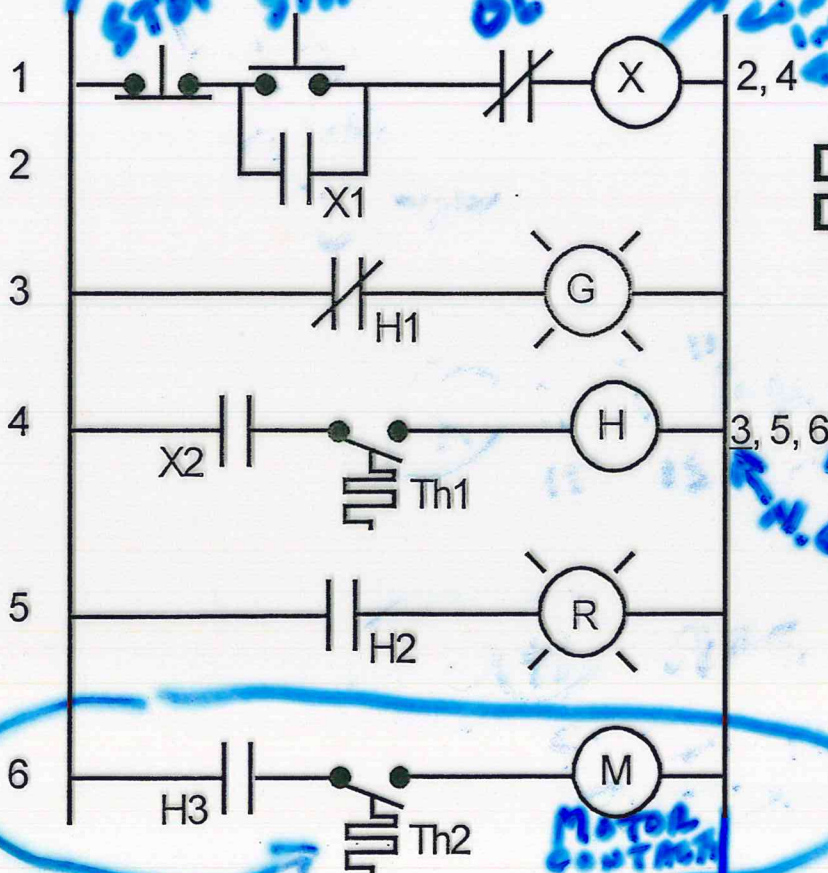

Draw Ladder Diagram:

Slide 16 of 17

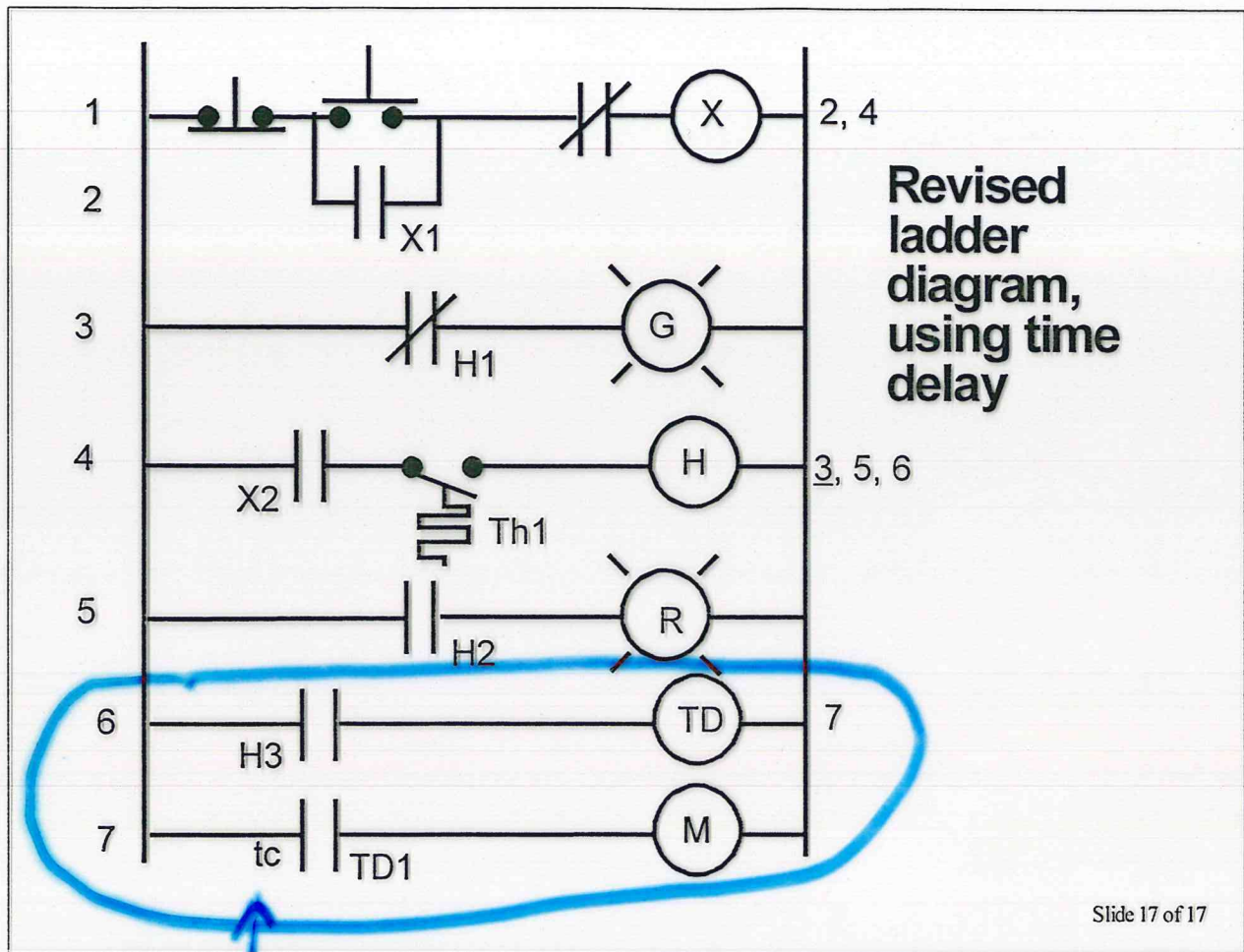

N.D.
TIME
TO
CLOSE

(X) IS A "RELAY" SINCE
IT IS A CONTROL
DEVICE

(M), (H) ARE "LOADS"
SINCE THEY ARE
POWER DEVICES
(AND CONTROL
DEVICES)