
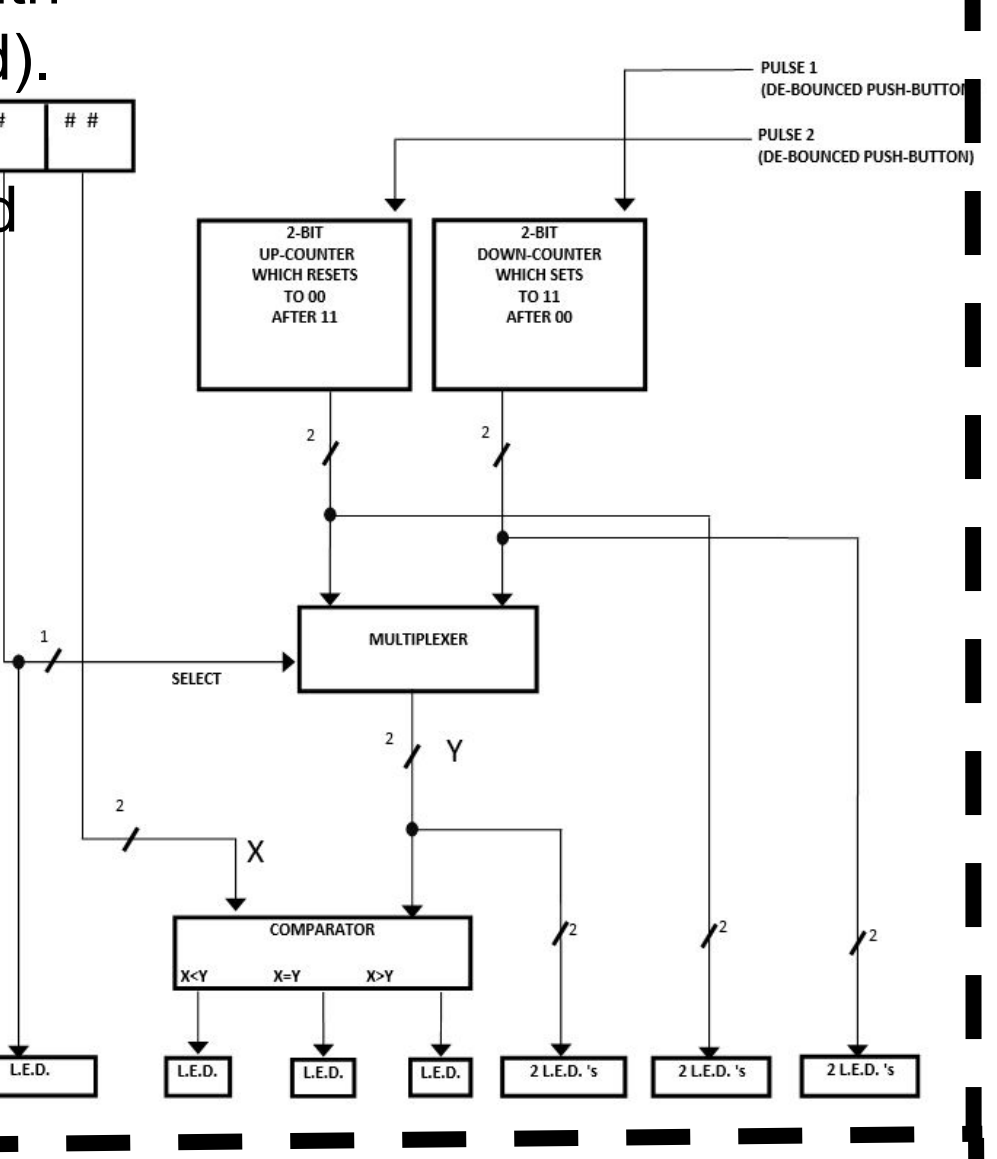


Lab 2: Beginning Computer Instruction-Set Design and PLC Equivalent Processing


 
1. A Logisim circuit simulation using only FLIP-FLOP's, INVERTORS, AND's, OR's, and NAND's for all circuits
2. TTL SSI chips on circuit trainers using only FLIP-FLOP's, INVERTORS, AND's, OR's, NAND's for all circuits. Also implement all 10 LED's (extra LED's are in stock, and resistors too, if needed)
3. NanoLC Programmable Logic Controllers (PLC's) with improvised inputs and outputs (debouncing not required). You may encode your inputs and outputs and use the display screen on the base unit; You may also input and output an encoded serial bit stream if you run out of parallel ways to input and output everything.



Lab 6/7/8: Vector-Array / Neuron Processor Design

1. Create four parallel scalar functional units with vector registers V_i, V_j, V_k created from R_i, R_j, R_k of the units.
2. Add a 32-bit adder to add the two 16-bit product results from each unit after a vector multiply, as part of a matrix row x column instruction
3. Put results into a 32 bit scalar accumulator, then into a neuron transfer function.
4. Create an embedded code stack, controlled by a program counter via a master control unit with a final state machine that implements the simple pipeline of fetch, decode, execute, and write-back; plus any special states.
5. Then embed a carefully crafted assembly language code segment to demonstrate the functionality of your instruction set and circuitry in the minimal amount of time that you can defend as providing comprehensive testing of all scalar, vector, matrix, and neuron machine instructions and hardware.

- 5 Main
- 3 Master Control
- 3 Control Logic
- 1 Parallel Scalar
- 2 Neuron Transfer Function
- 5 Execute Step
- 4 Register Bank
- 4 Status Register




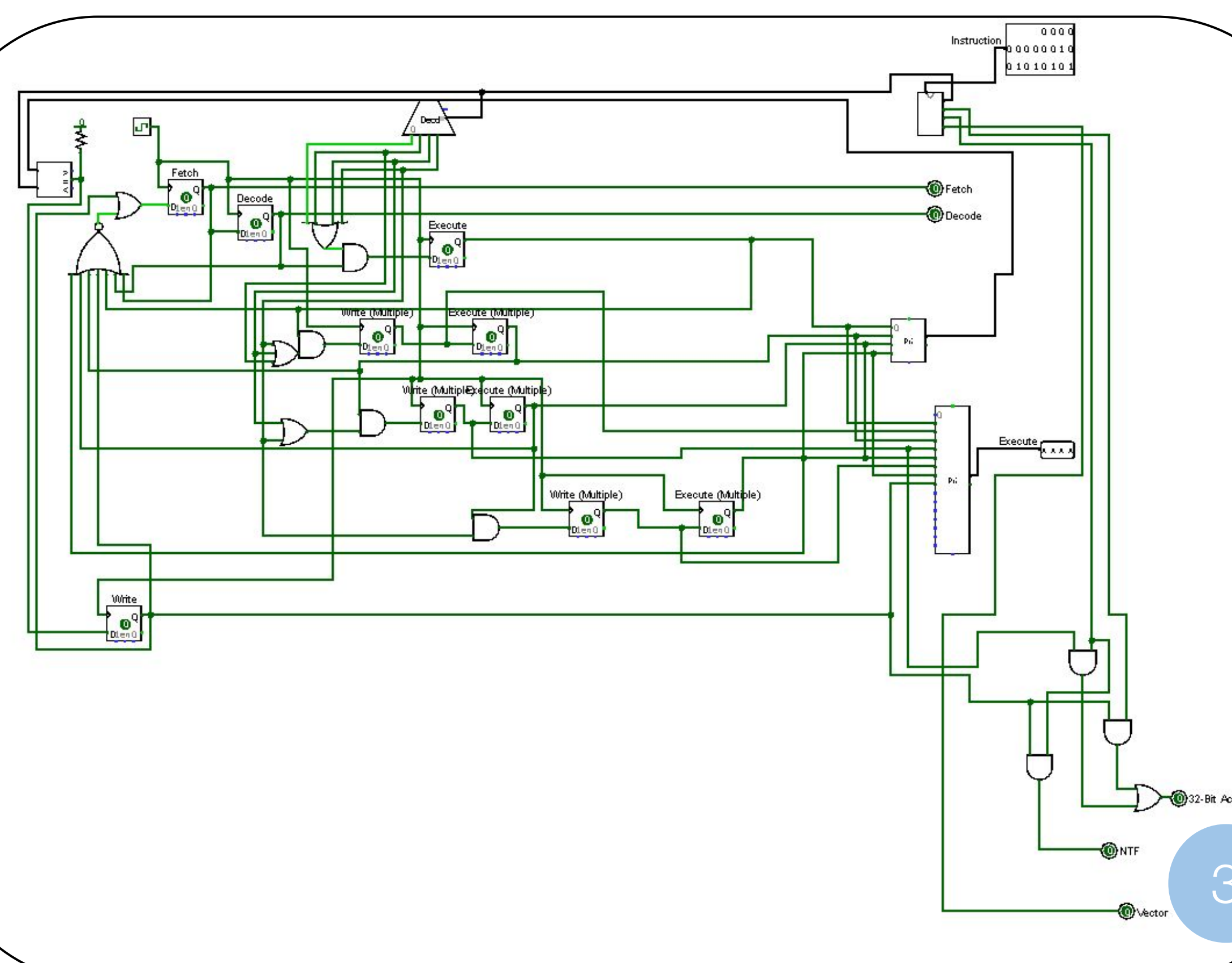
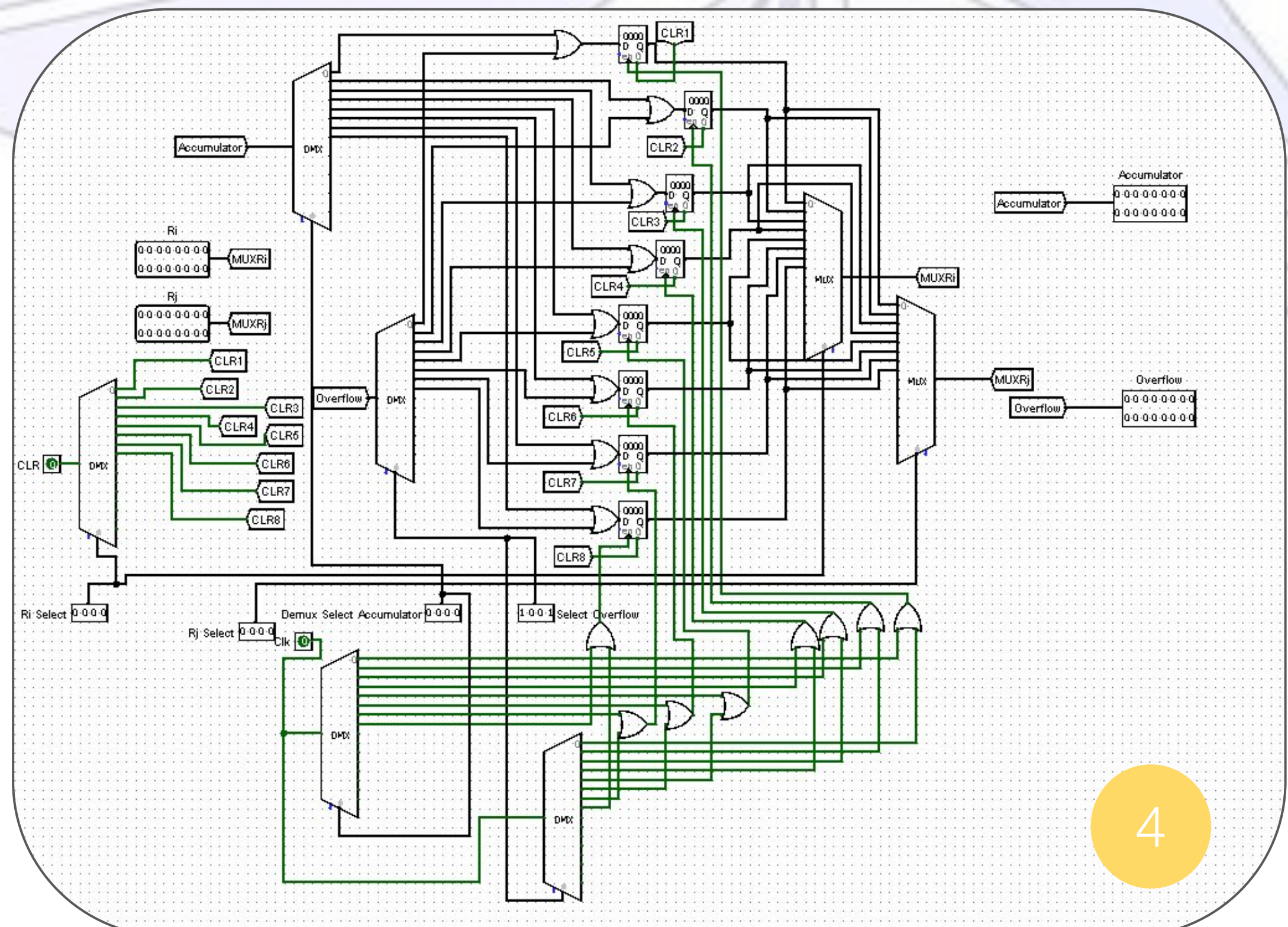


Lab 3: Computer Instruction-Set Design continued, including FPGA; Plus PLC Power-Control

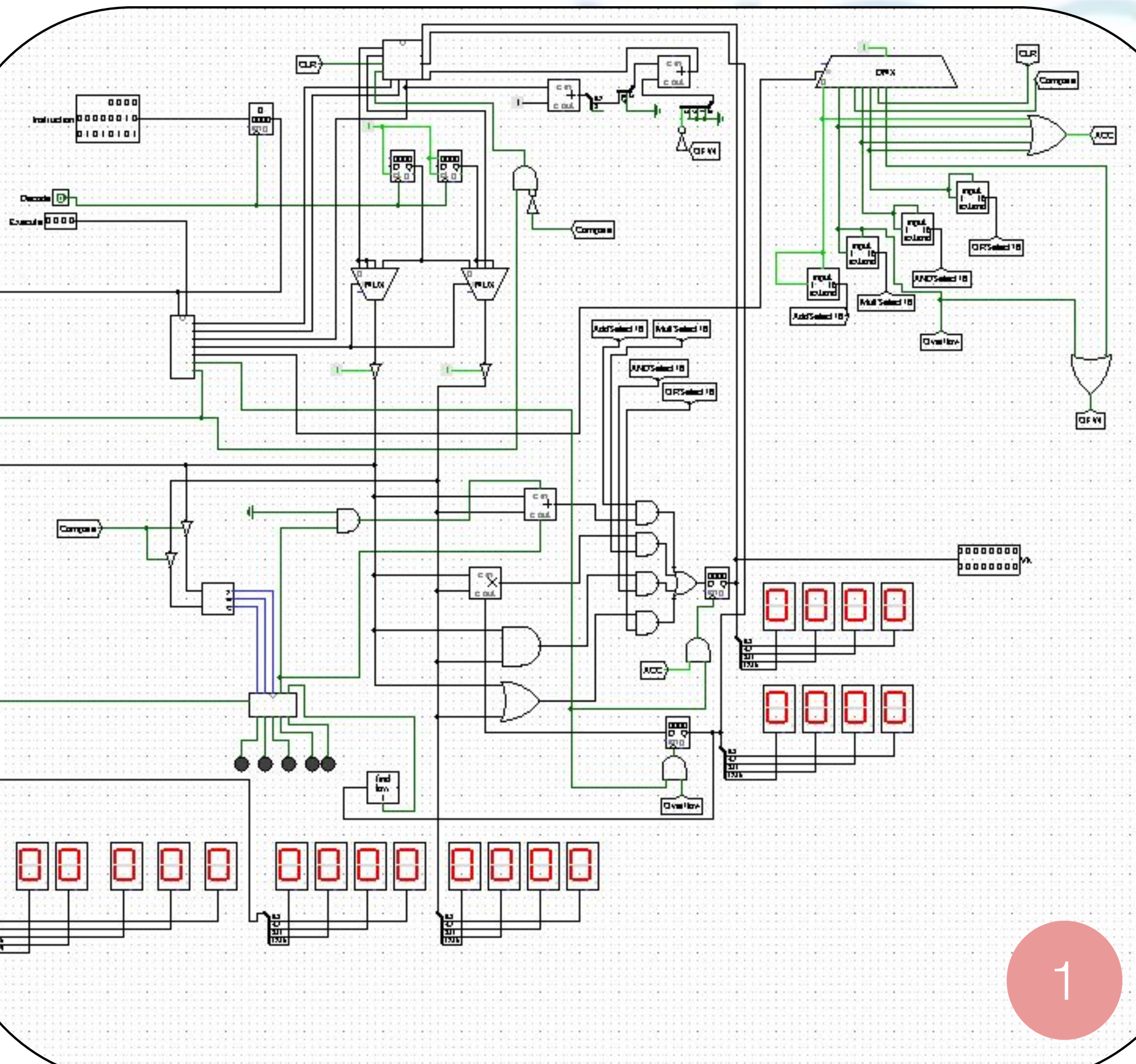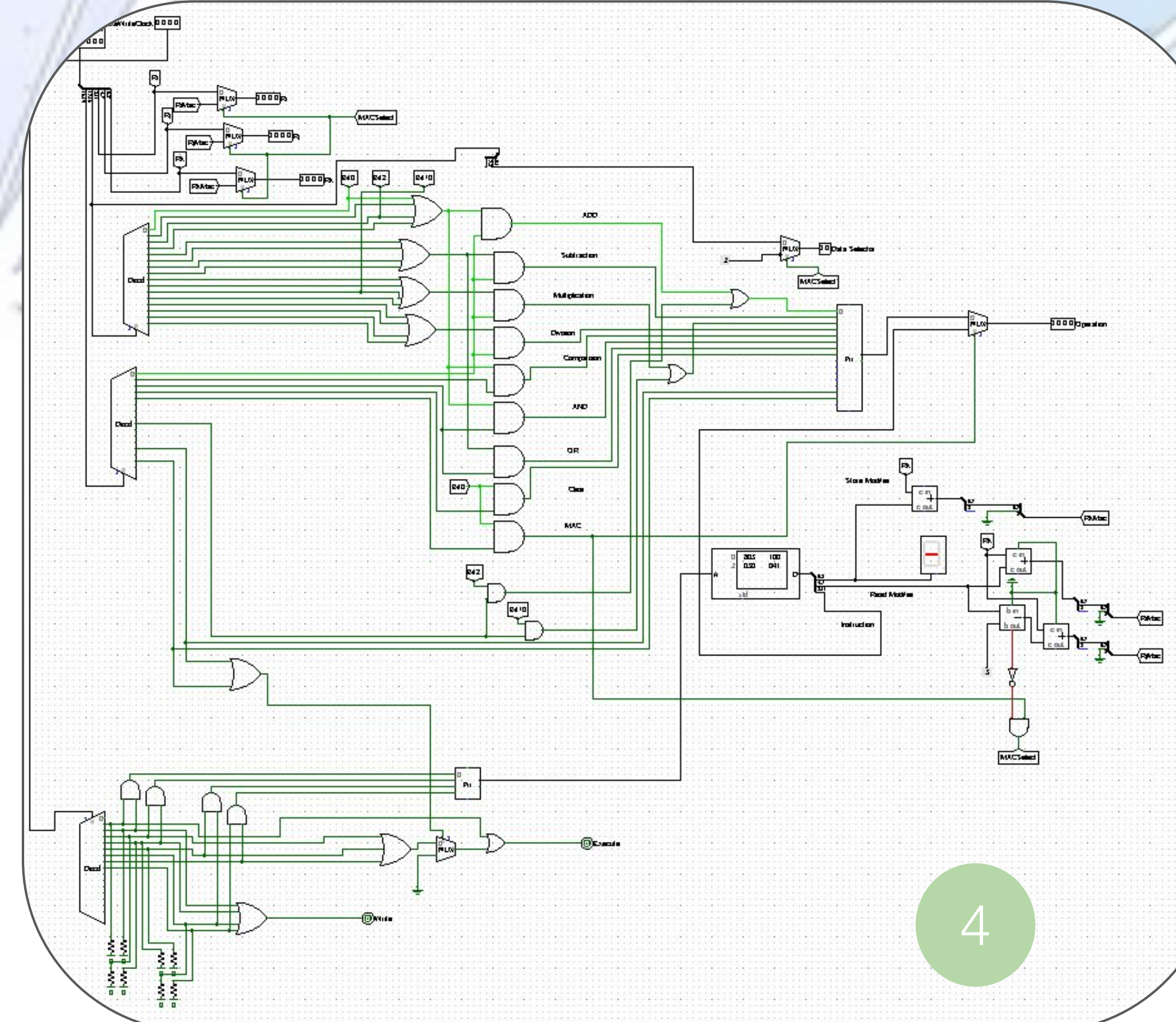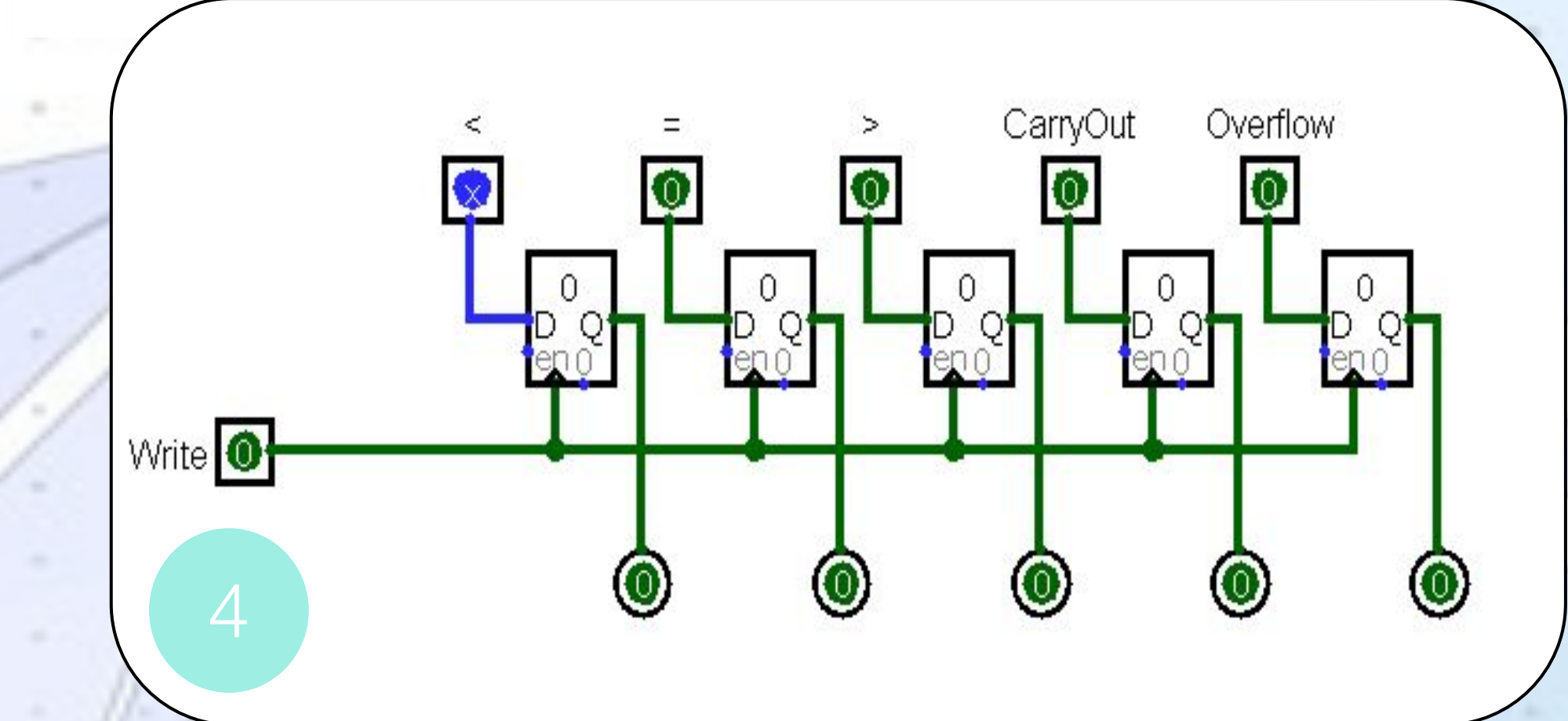 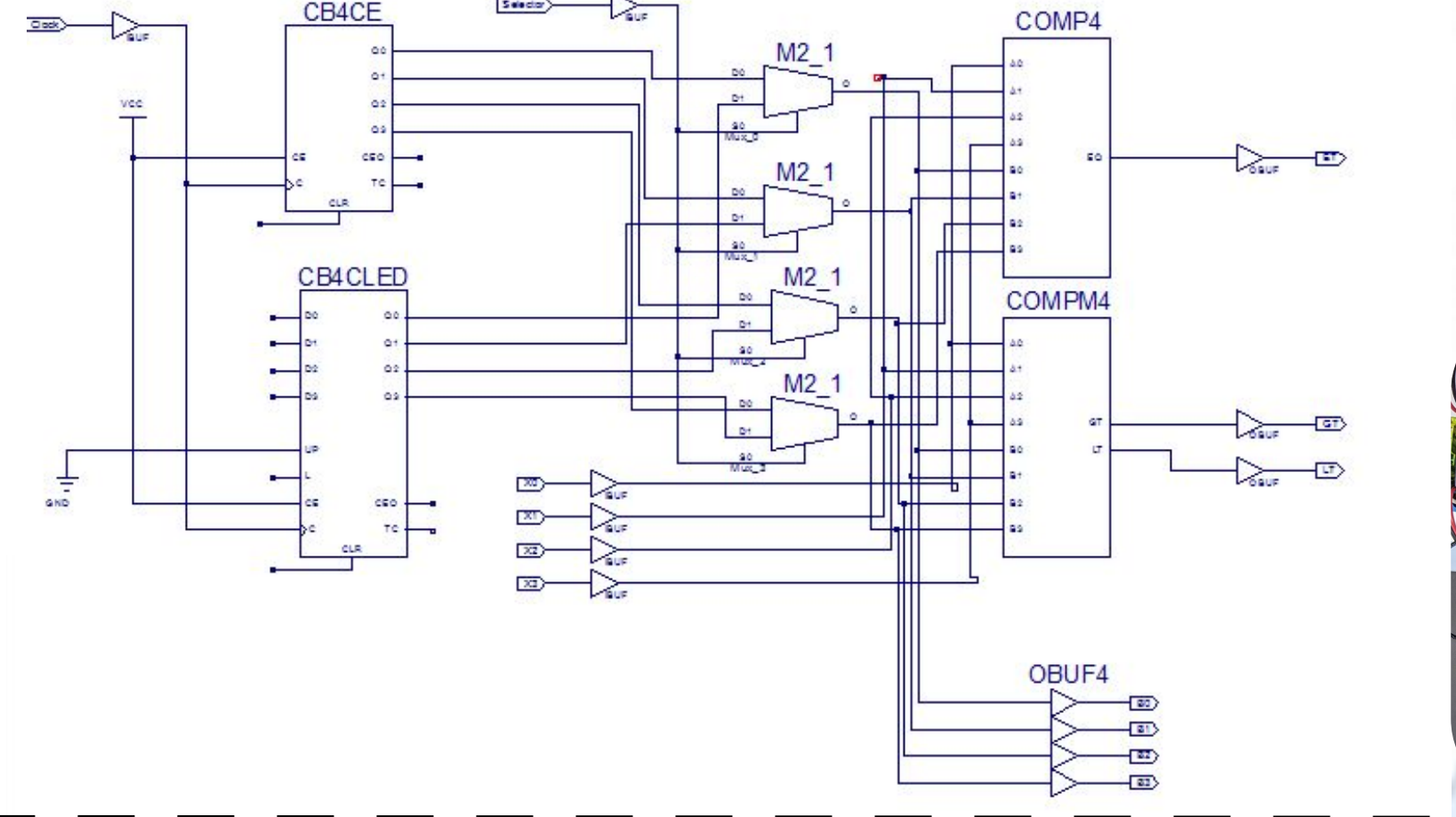1. Using a NanoLC PLC Base Unit, I/O unit, and Relay, turn on a 120 volt light bulb five seconds after an external input pushbutton is pressed.
2. Design and implement the circuit below in two ways:
 - A Logisim circuit simulation using only FLIP-FLOP's, INVERTORS, AND's, OR's, and NAND's for all circuits
 - Field Programmable Gate Array (FPGA) using the largest functional blocks possible (I.e, avoid using only FLIP-FLOP's, INVERTORS, AND's, OR's, and NAND's)

Lab3 Opcode: Instruction Set:

- (OP-CODE=1): Compare operand to up-counter count
- (OP-CODE=0): Compare operand to down-counter count




Lab 5 Computer Instruction-Set Design continued with 2-way superscalar pipelines, including FPGA; Plus Advanced \$5000 Phoenix Contact PLC's





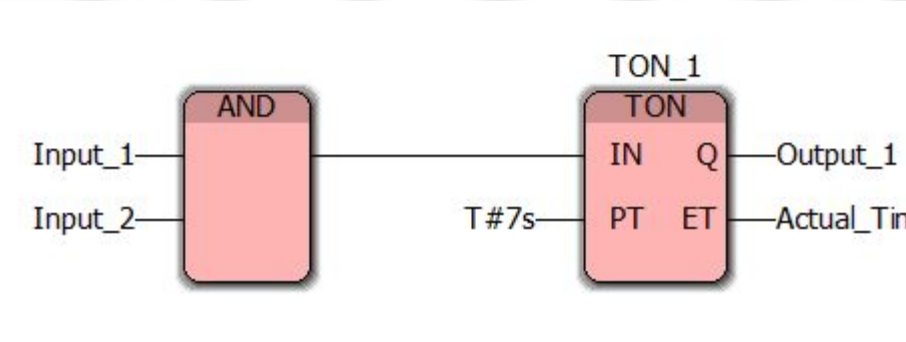
1. Using an Advanced AXC/AXL PLC, perform the lab experiment shown in our custom Lab Manual and include in report info you recommend be added to this manual
2. Duplicate everything done below in the last lab. You will be creating two parallel pipelines in a 2-way Superscalar architecture. Create a STACK of all 13 instructions of your instruction set, and create a FINITE STATE MACHINE that alternates FETCHING sequential instructions from your stack, alternating which pipe receives the instruction. Let hardware DECODE and EXECUTE as in last lab. NOTE: This architecture is pipelined and not yet fully superscalar since FETCHES are not yet done simultaneously.

Instruction Set

- DON'T CHANGE THE OP-CODES !
- AND TURN OFF OPERATIONS THAT ARE NOT
- OP-CODE = 0000 Add Immediate Data to counter #1 (UP-COUNTER)
 - OP-CODE = 0001 Add Immediate Data to counter #2 (DOWN-COUNTER)
 - OP-CODE = 0010 Compare Immediate Data with counter #1 (UP-COUNTER)
 - OP-CODE = 0011 Compare Immediate Data with counter #2 (DOWN-COUNTER)
 - OP-CODE = 0100 AND Immediate Data to counter #1 (UP-COUNTER)
 - OP-CODE = 0101 AND Immediate Data to counter #2 (DOWN-COUNTER)
 - OP-CODE = 0110 OR Immediate Data to counter #1 (UP-COUNTER)
 - OP-CODE = 0111 OR Immediate Data to counter #2 (DOWN-COUNTER)
 - OP-CODE = 1000 Add Counters
 - OP-CODE = 1001 Compare Counters
 - OP-CODE = 1010 AND Counters
 - OP-CODE = 1011 OR Counters
 - OP-CODE = 11XX Turn off everything but display of Op-code and Operand



Symbol/...	BOOL	Data Type	Process Data Item
Input_1	BOOL	# 1 AXL F DI 16/1 1H \ IN00	
Input_2	BOOL	# 1 AXL F DI 16/1 1H \ IN01	
Actual_Ti...	TIME		
Output_1	BOOL	# 2 AXL F DO 16/1 1H \ O...	

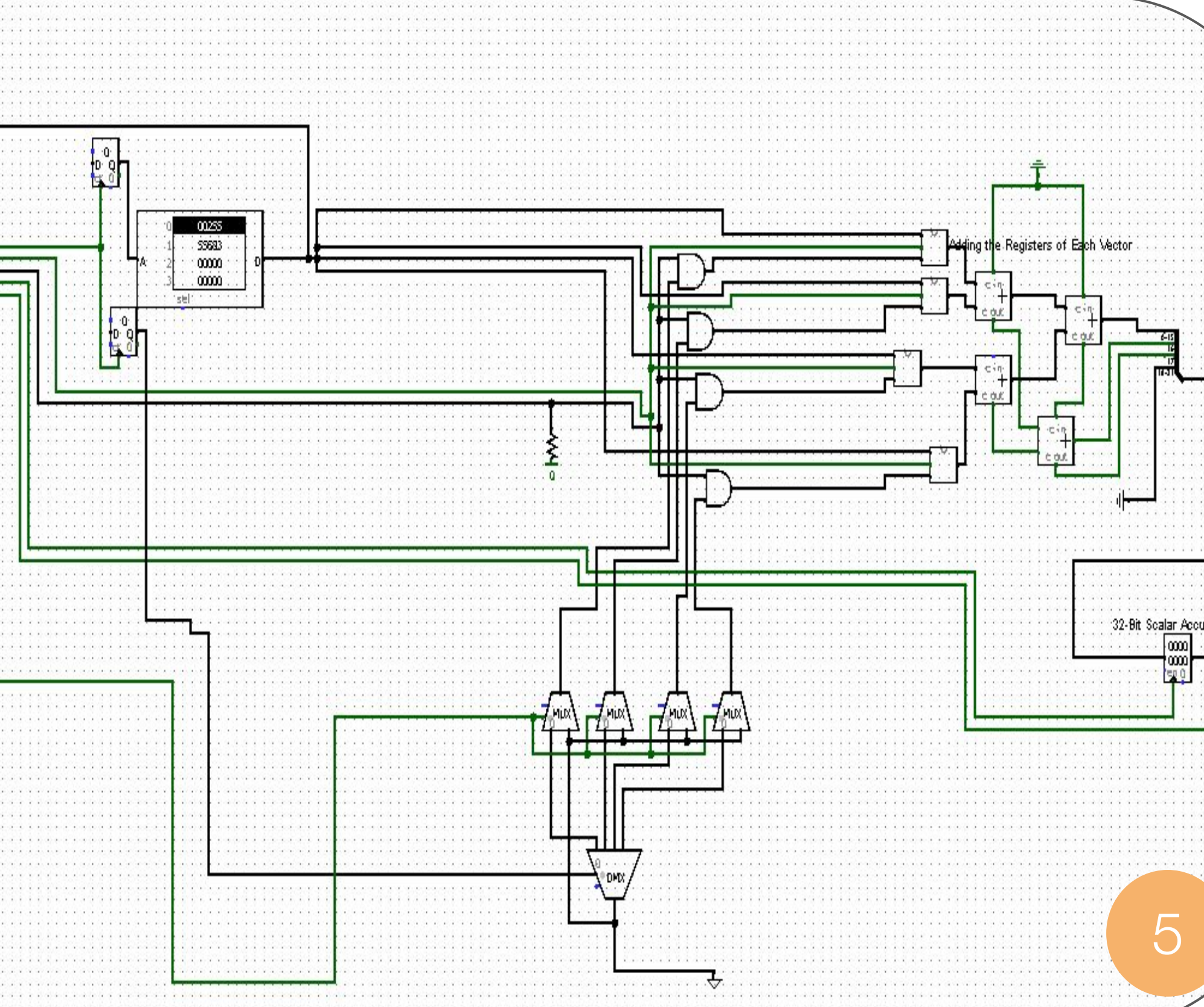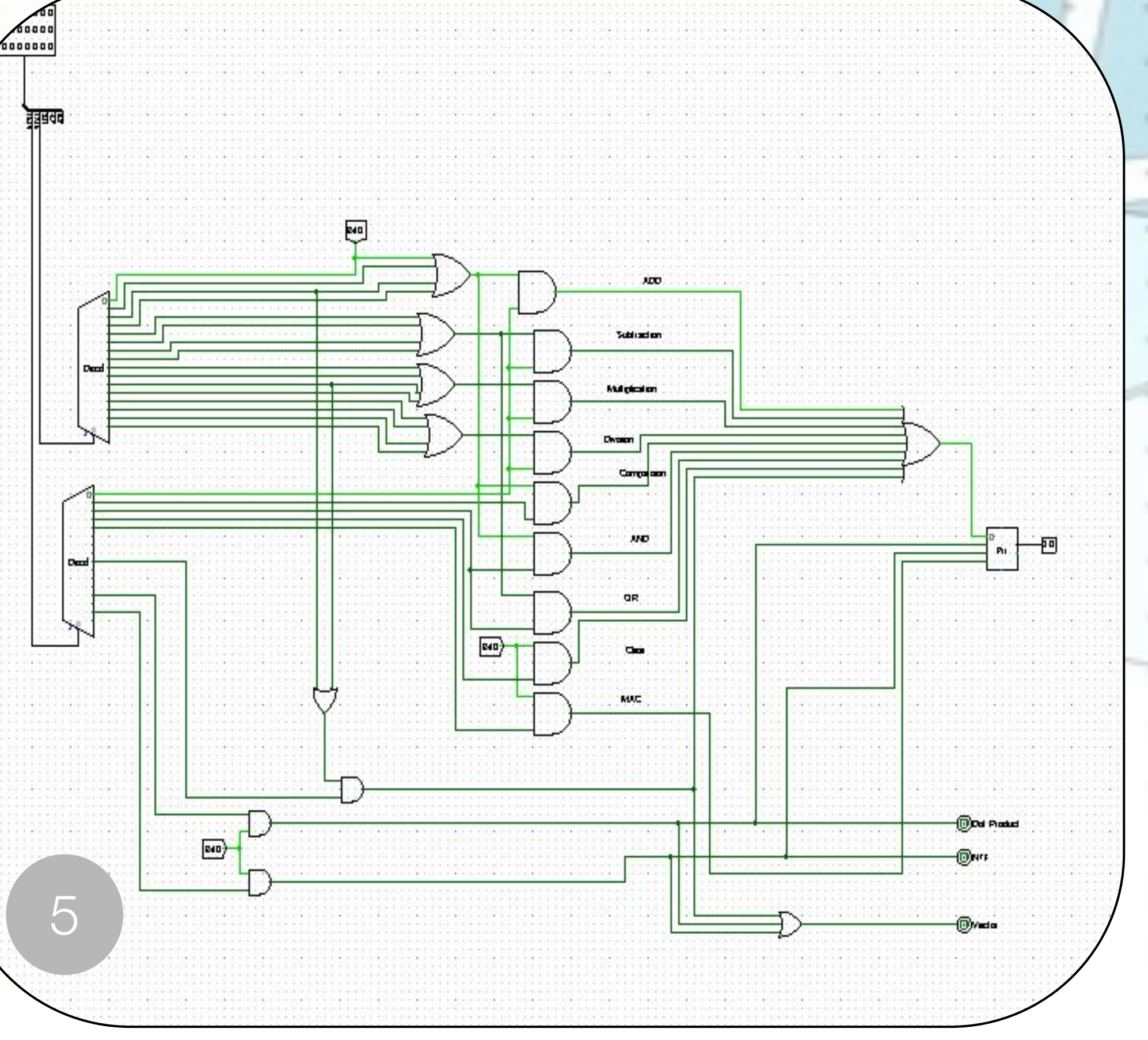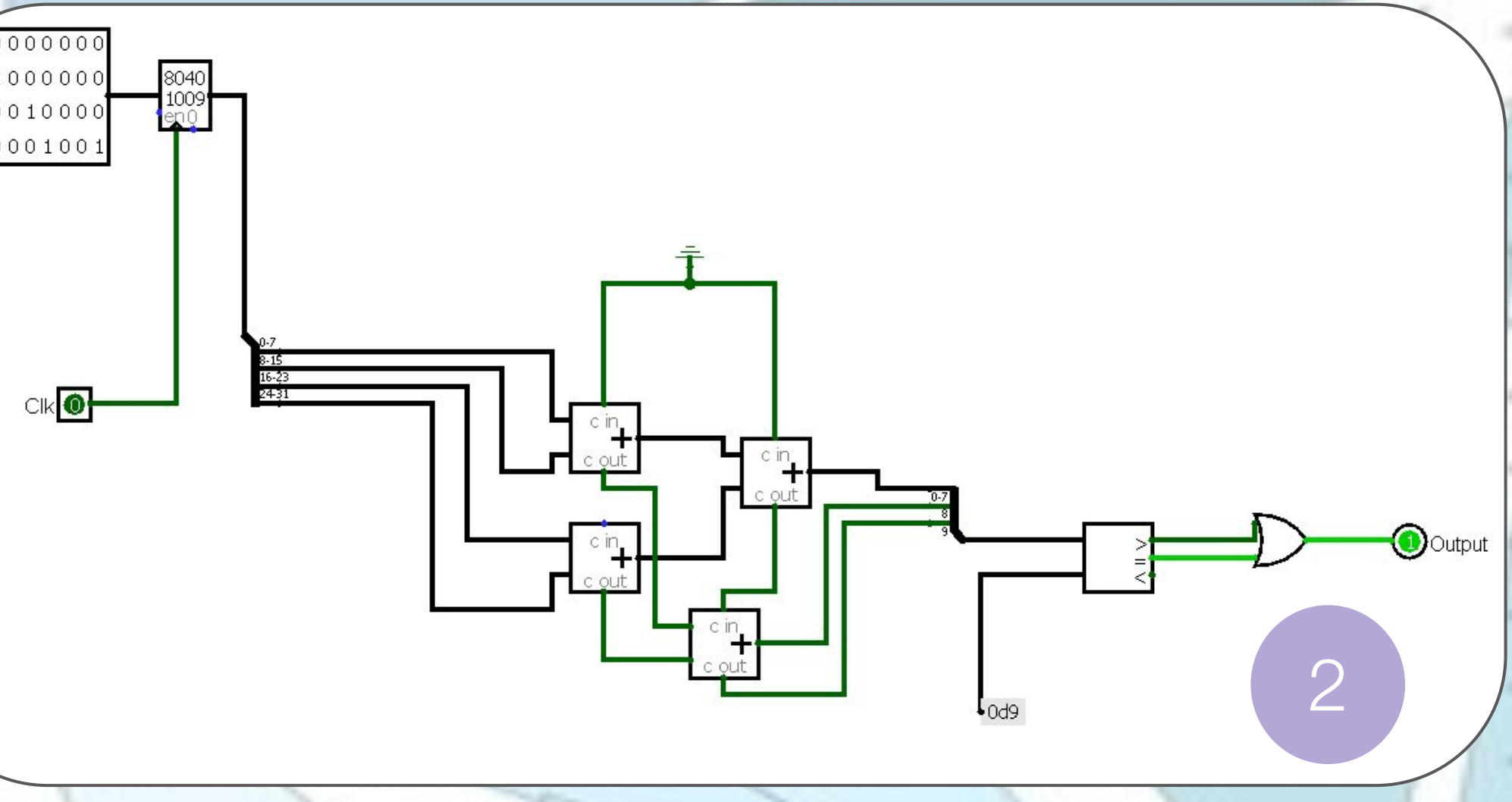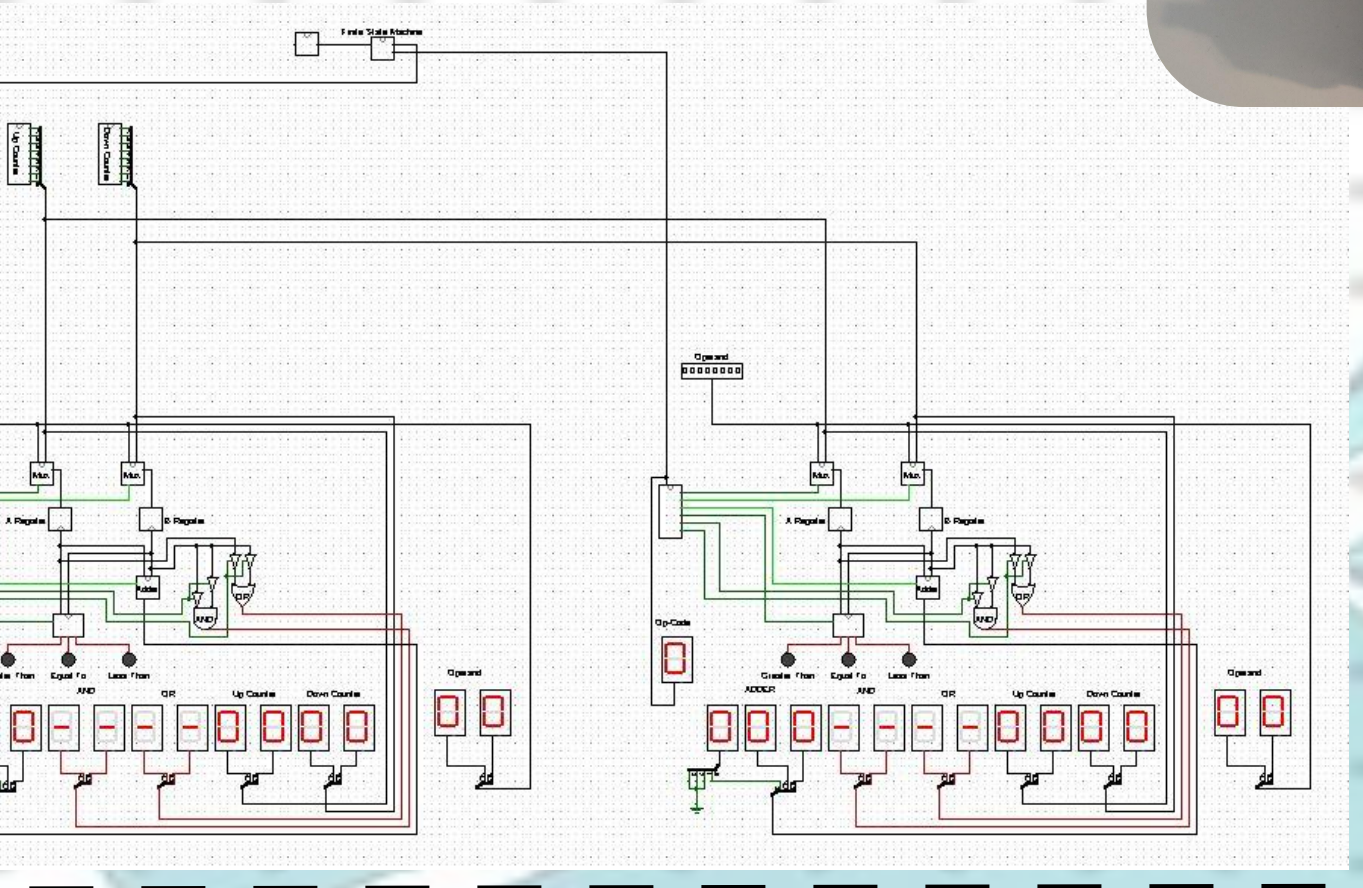 

MACHINE INSTRUCTION SET

SCALAR ARITHMETIC ADDITION

00h (OP-CODE = 00000000) Ri + counter#1 →Rk
 01h (OP-CODE = 00000001) Ri + counter#2 →Rk
 02h (OP-CODE = 00000010) Ri + Rj →Rk
 03h (OP-CODE = 00000011) counter#1 + counter#2 →Rk

SCALAR ARITHMETIC SUBTRACTION

04h to 07h (OP-CODE = 000011XX) Reserved for subtraction instructions

SCALAR ARITHMETIC MULTIPLICATION

08h (OP-CODE = 00001000) Ri x counter#1 →Rk, overflow →Rk+1 (wrap to R0)
 09h (OP-CODE = 00001001) Ri x counter#2 →Rk, overflow →Rk+1 (wrap to R0)
 0Ah (OP-CODE = 00001010) Ri x Rj →Rk, overflow →Rk+1 (wrap to R0)
 0bh (OP-CODE = 00001011) counter#1 x counter#2 →Rk, overflow →Rk+1 (wrap to R0)

SCALAR ARITHMETIC DIVISION

0Ch to 0Fh (OP-CODE = 000011XX) Reserved for division instructions

SCALAR ARITHMETIC COMPARISON

10h (OP-CODE = 00010000) Compare Ri with counter#1 →Rk
 11h (OP-CODE = 00010001) Compare Ri with counter#2 →Rk
 12h (OP-CODE = 00010010) Compare Ri with Rj →Rk
 13h (OP-CODE = 00010011) Compare Counters

SCALAR LOGICAL AND

20h (OP-CODE = 00100000) Ri AND counter#1 →Rk
 21h (OP-CODE = 00100001) Ri AND counter#2 →Rk
 22h (OP-CODE = 00100010) Ri AND Rj →Rk
 23h (OP-CODE = 00100011) AND counters →Rk

SCALAR LOGICAL OR

24h (OP-CODE = 00100100) Ri OR counter#1 →Rk
 25h (OP-CODE = 00100101) Ri OR counter#2 →Rk
 26h (OP-CODE = 00100110) Ri OR Rj →Rk
 27h (OP-CODE = 00100111) OR counters →Rk

CLEAR

30h (OP-CODE = 00110000) Clear Ri

MAC
 (Multiply, Accumulate, Accumulator = Accumulator + (Ri x Rj) considering overflow also)

40h (OP-CODE = 01000000) Step 1: Accumulator →Rk+3 (wrap to R0+)
 Step 2: Overflow →Rk+4 (wrap to R0+)
 Step 3: Ri x Rj →Rk, overflow →Rk+1 (wrap to R0)
 Step 4: (Rk+3)+Rk →Rk
 Step 5: (Rk+4)+(Rk+1)+Carry →Rk+1

VECTOR-ARRAY / MATRIX & NEURON INSTRUCTIONS

V_i, V_j , and V_k are created from R_i 's, R_j 's, and R_k 's of the four parallel functional units

VECTOR ARITHMETIC ADDITION

82h (OP-CODE = 10000010) $V_i + V_j \rightarrow V_k$

VECTOR ARITHMETIC SUBTRACTION

84h to 87h (OP-CODE = 100001XX) Reserved for subtraction instructions

VECTOR ARITHMETIC MULTIPLICATION

0Ah (OP-CODE = 10001010) $V_i \times V_j \rightarrow V_k$, overflow →Rk+1 (wrap to R0)

VECTOR ARITHMETIC DIVISION

8Ch to 8Fh (OP-CODE = 100011XX) Reserved for division instructions

MATRIX ROW x COLUMN (i.e., Dot-Product)

C0h (OP-CODE = 11000000) $V_i \times V_j \rightarrow V_k$, overflow →Rk+1 (wrap to R0)
 $V_k(1)+V_k(2)+V_k(3)+V_k(4) \rightarrow$ 32-Bit Scalar Accumulator

NEURON TRANSFER FUNCTION

E0h (OP-CODE = 11100000) $V_i \times V_j \rightarrow V_k$, overflow →Rk+1 (wrap to R0)
 $V_k(1)+V_k(2)+V_k(3)+V_k(4) \rightarrow$ 32-Bit Scalar Accumulator
 32-Bit Scalar Accumulator → Neuron Transfer Function

EGCR433 Summary:Dillon Dotson (Senior Engineering), Patrick Durofchalk (Senior Computer Engineering), Miguel Gonzalez (Sophomore Computer Engineering)