

# Welcome to PHOENIX CONTACT

## Relays




January 30, 2009  
by Arnold Offner



# Relays

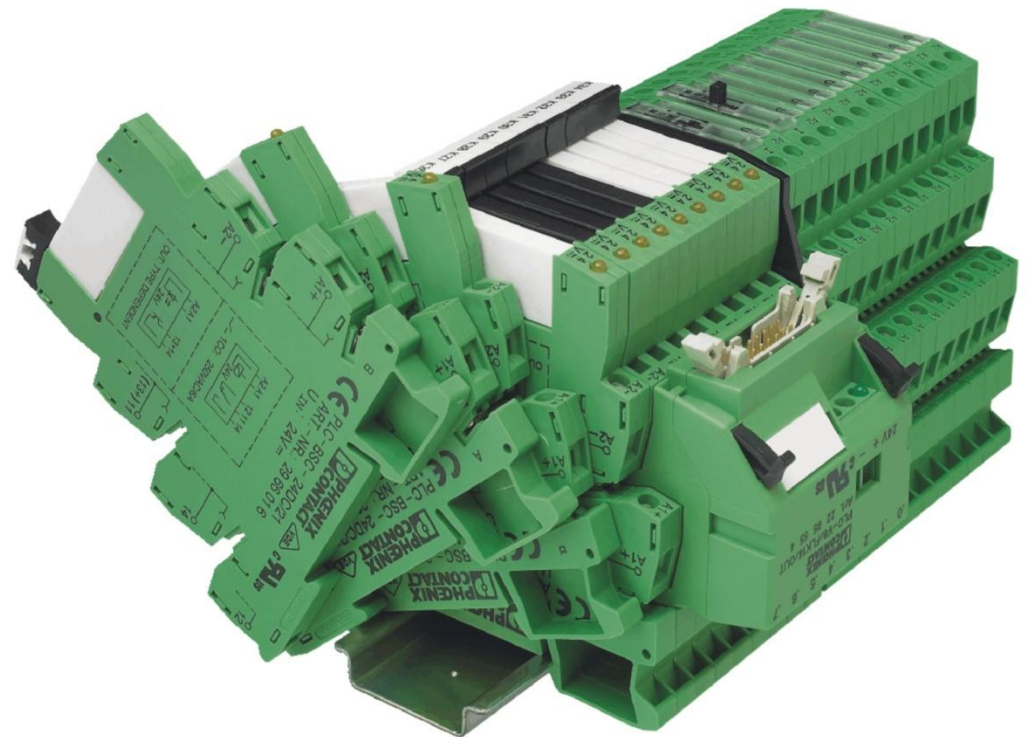
## Agenda

- Relay Types
- Basic Functionality
- Load Types
- Application Types



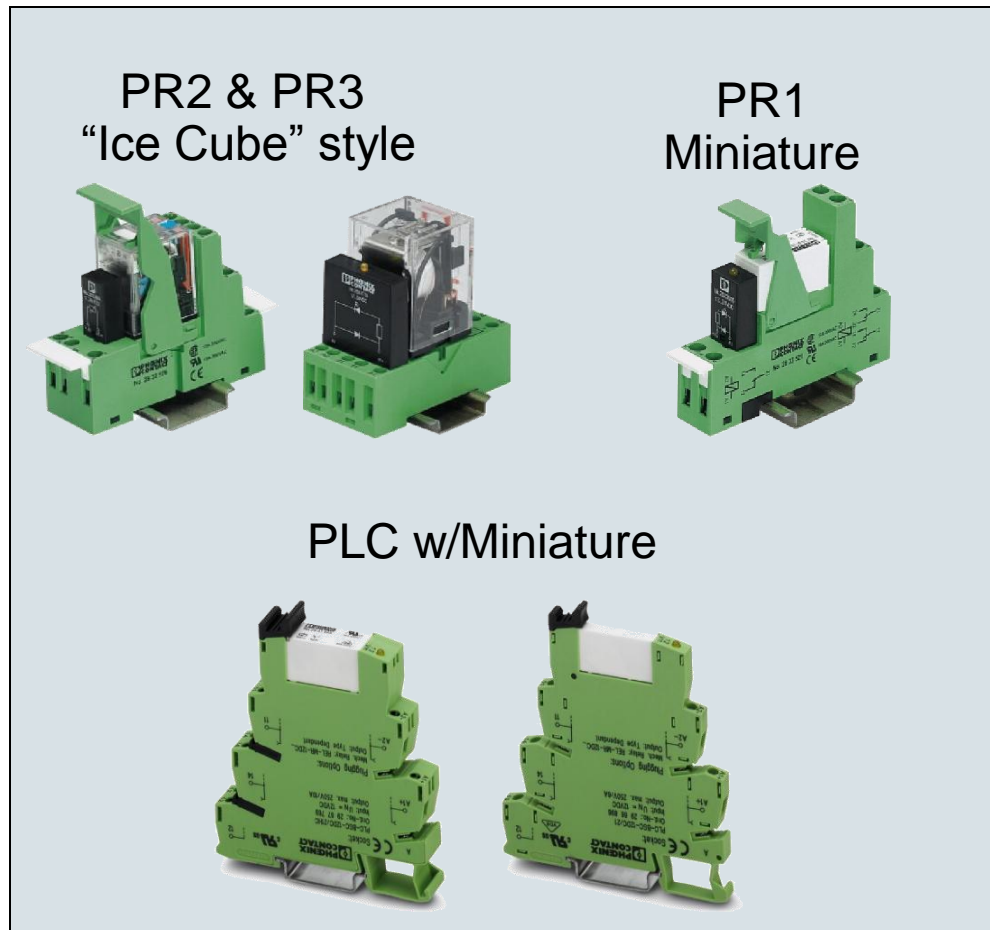
# Relay Types

- A switching device with moving contacts which are energized by a magnetic field.





## Electromechanical

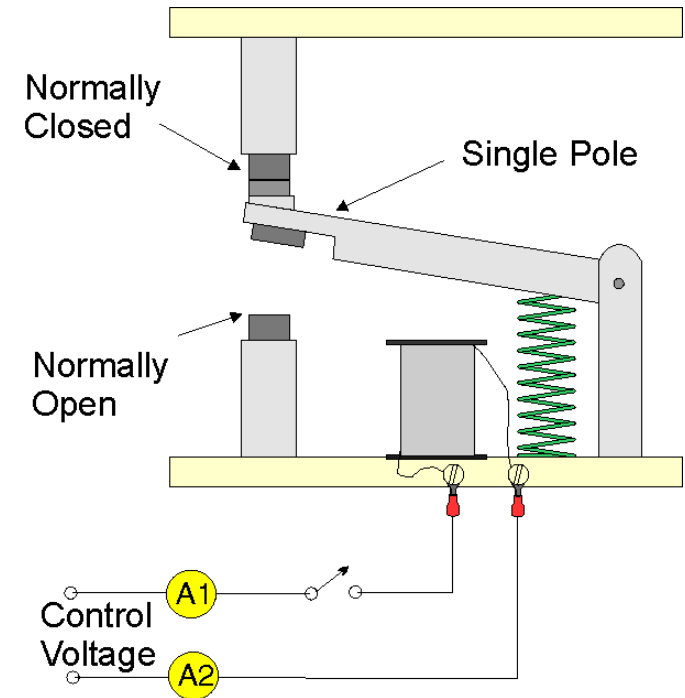

# Relay Types




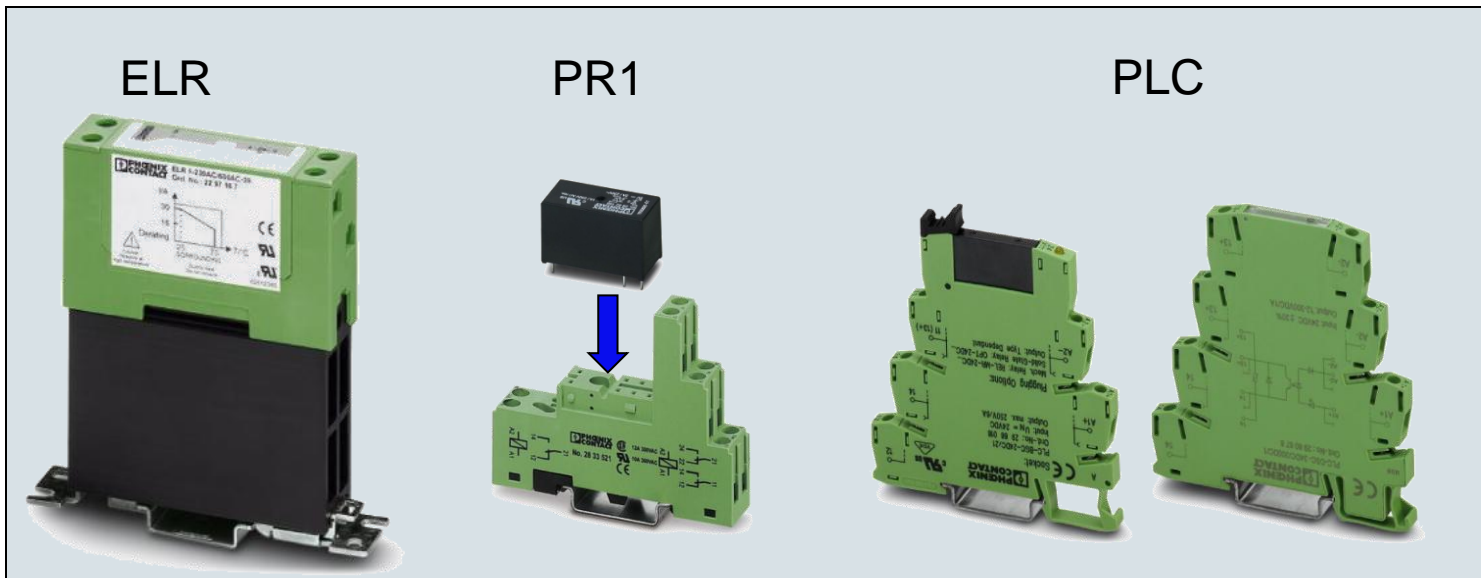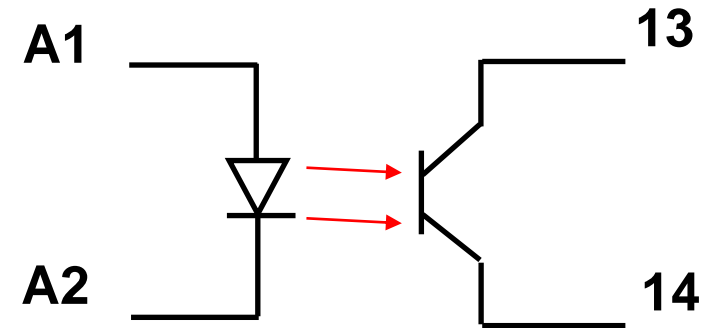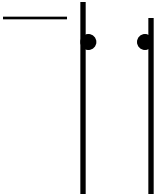
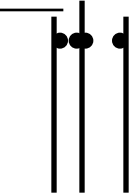
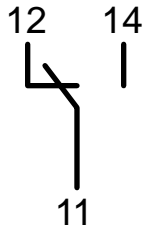
- A switching device with no contacts (moving parts) and switches entirely by electronic means.

## Solid State



# Relay Types

## Contact types

Designation	Number Designation	Contact Picture	Schematic Symbol
Normally Open NO (Form A)	1		
Normally Closed NC (Form B)	2		
Single Pole Double Throw SPDT (Form C)	21		

# Relay Types

## Contact types


- Single pole, double throw

(SPDT)




- Double pole, double throw

(DPDT)

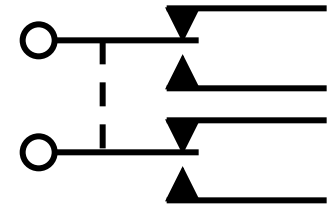

- Three pole, double throw

(3PDT)

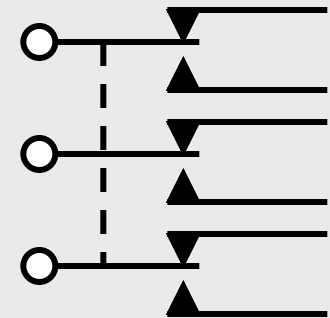

# Relay Types

## Technical and economic comparison: Electromechanical vs. Solid State Relay

Criteria	SSR	EMR
Switching of different loads (AC/DC)	--	+
Switching capacity DC load	+	+
Switching capacity AC load	-	++
Switching frequency	++	--
Vibration and shock resistance	++	o
Reliability	++	+
Electrical service life	++	- ... +
Costs	-	+
Power dissipation / heating	-	+
Electrical isolation in the output	--	++
Contact bouncing	++	--


 Advantage

 Disadvantage


# Basic Functionality

## Electromechanical

Relay - An Electrically Actuated Switch

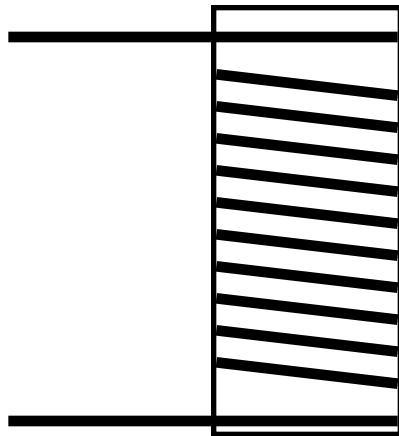

Coil

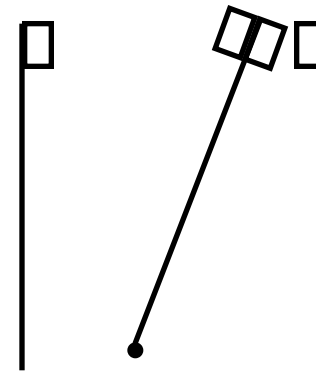


Contacts



# Basic Functionality


# Electromechanical

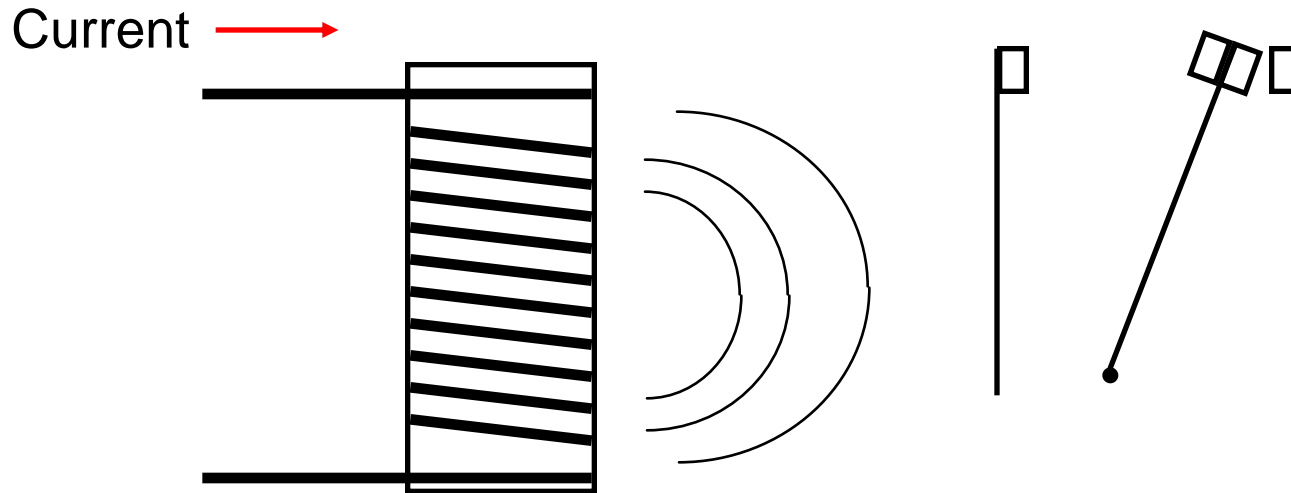

Current through the coil produces a magnetic field.

# Basic Functionality

## Electromechanical

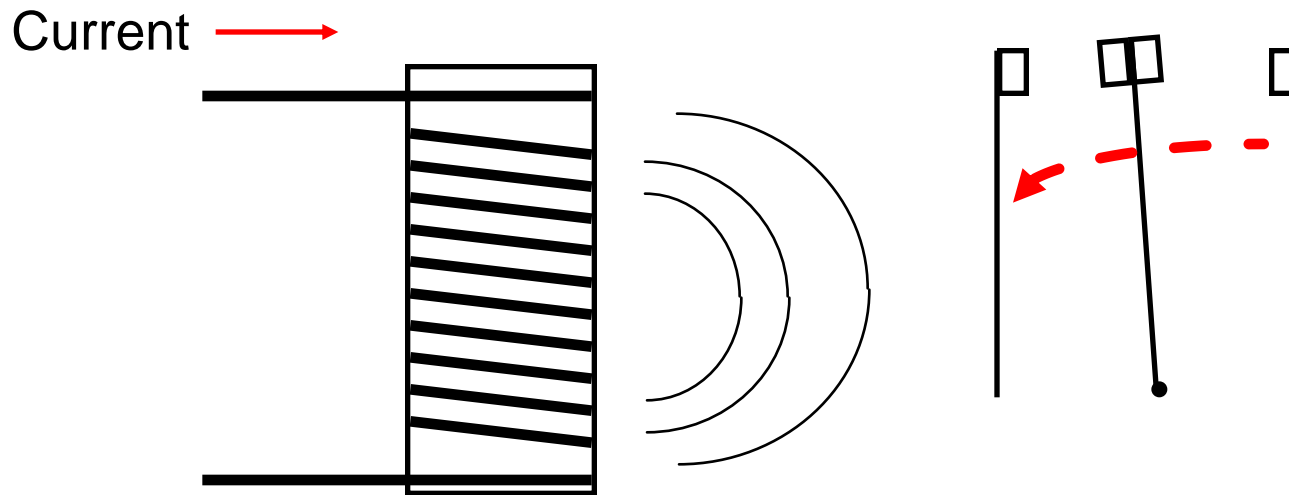


Magnetic force pulls on the moving contact causing it to change states.

# Basic Functionality

# Electromechanical

Coil Inductive Kickback


No Current

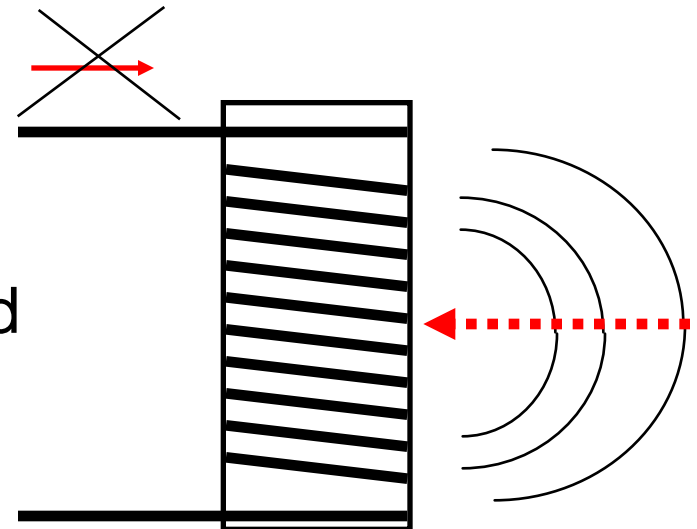

The relay coil is an inductive load for the driving device

# Basic Functionality

# Electromechanical

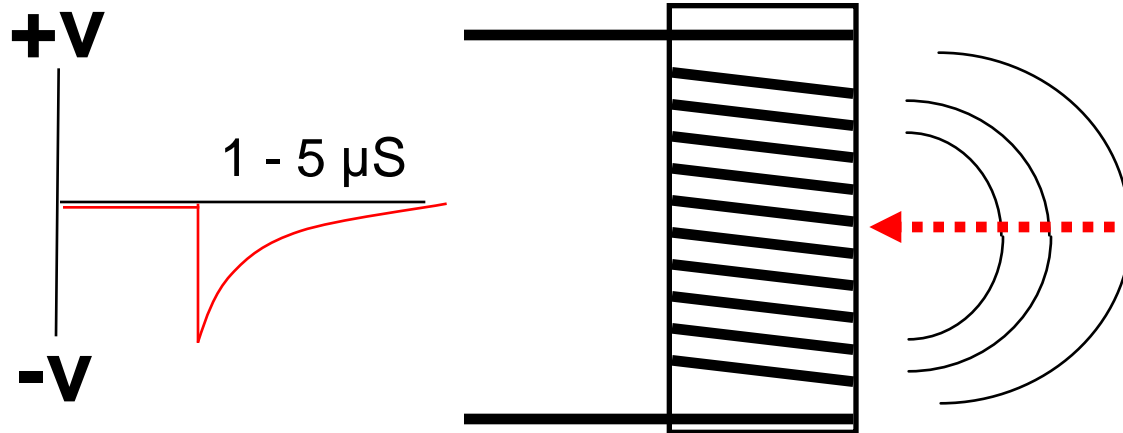


The collapsing magnetic field causes a high voltage spike on the coil.

# Basic Functionality

# Electromechanical

Protect the controls !

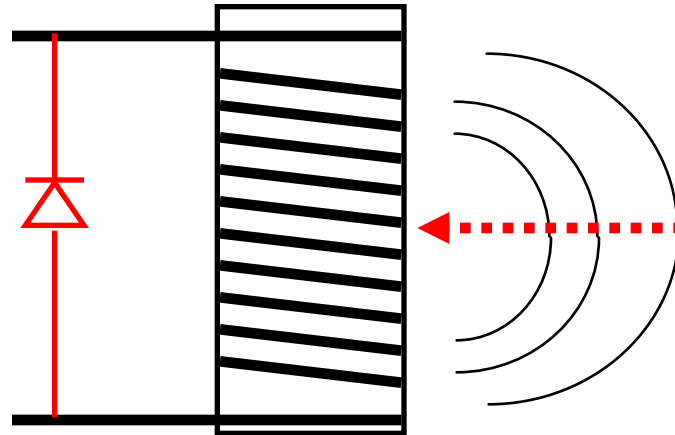


# Basic Functionality





Electromechanical

Protect the Coil !


Polarity Protection

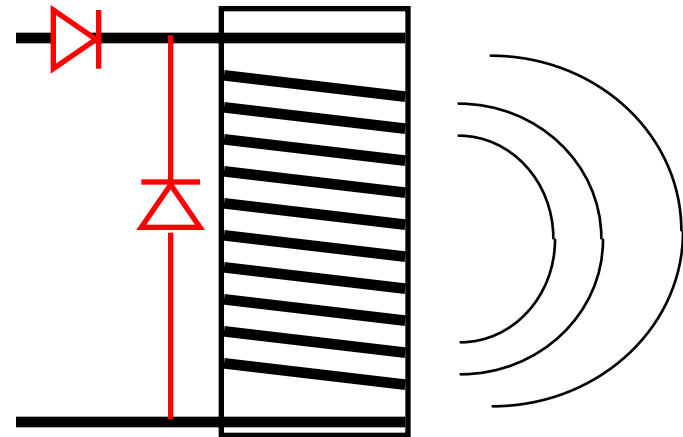

# Inductive Kickback

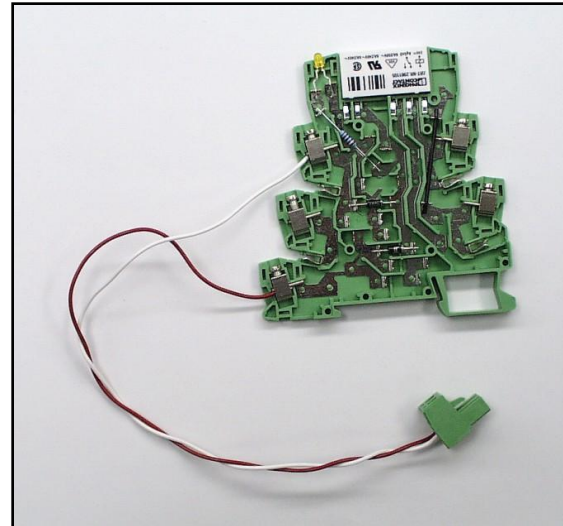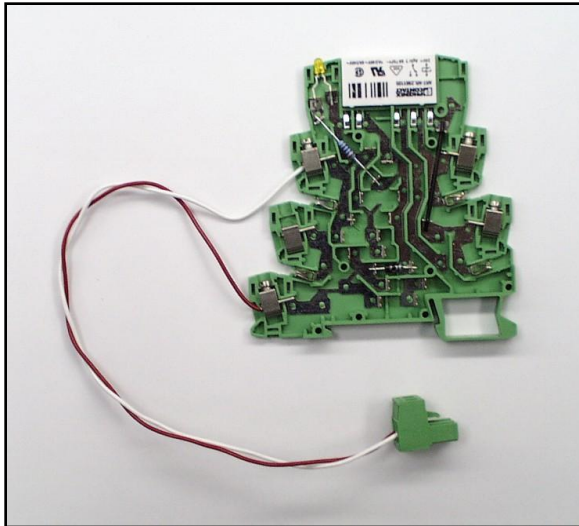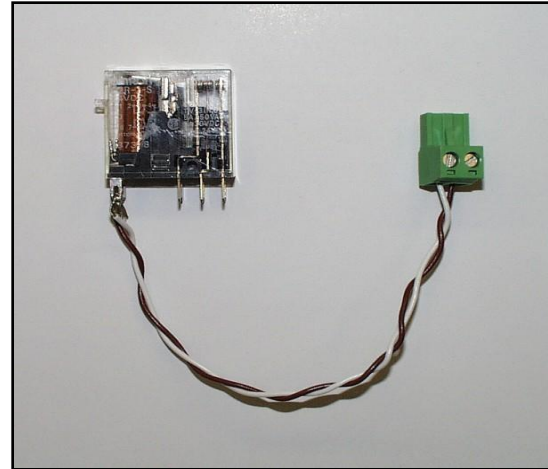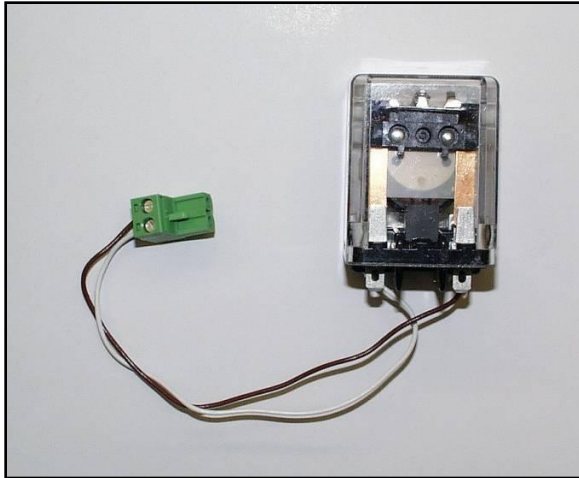


Tek **Stop** Single Seq 10.0kS/s

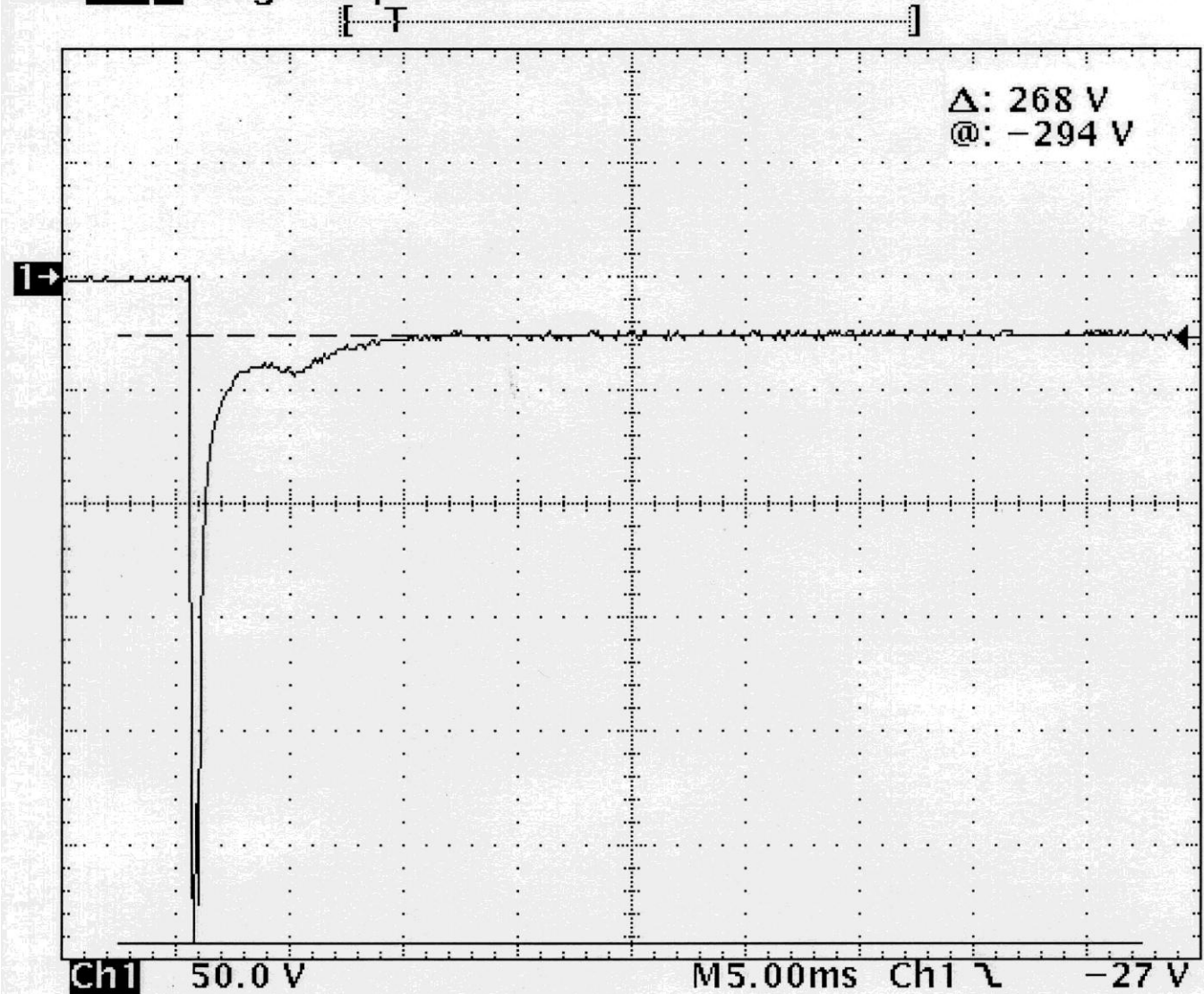

P&B KUEP-3D15-24 Ice cube style relay




Tek **stop:** Single Seq\_ 10.0kS/s

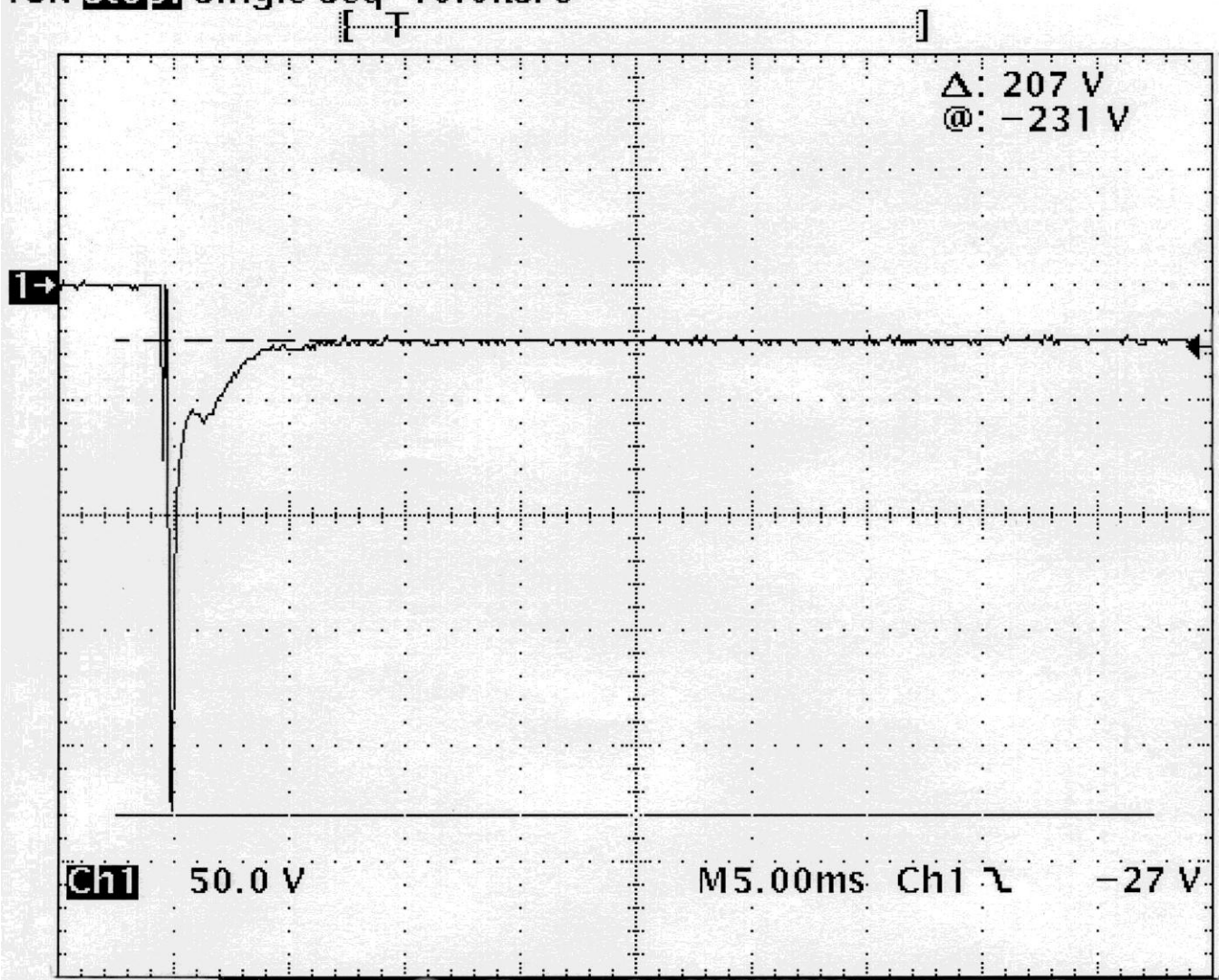

Omron G2R-2-S 24DC Ice cube style relay


Tek **Stop:** Single Seq 10.0kS/s

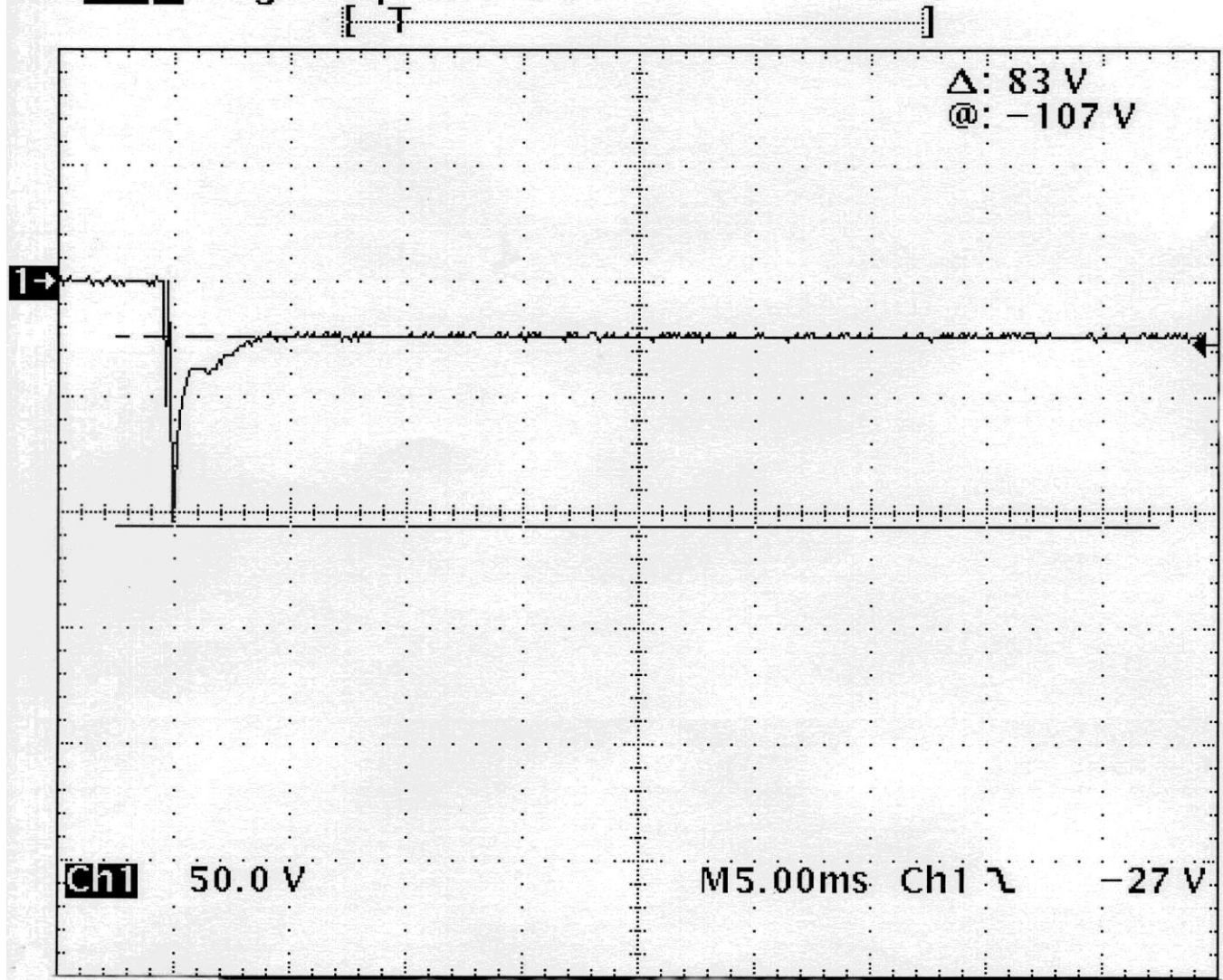

PLC-RSC-24DC/21 w/o inductive kickback diode



Tek **Stop:** Single Seq 10.0kS/s

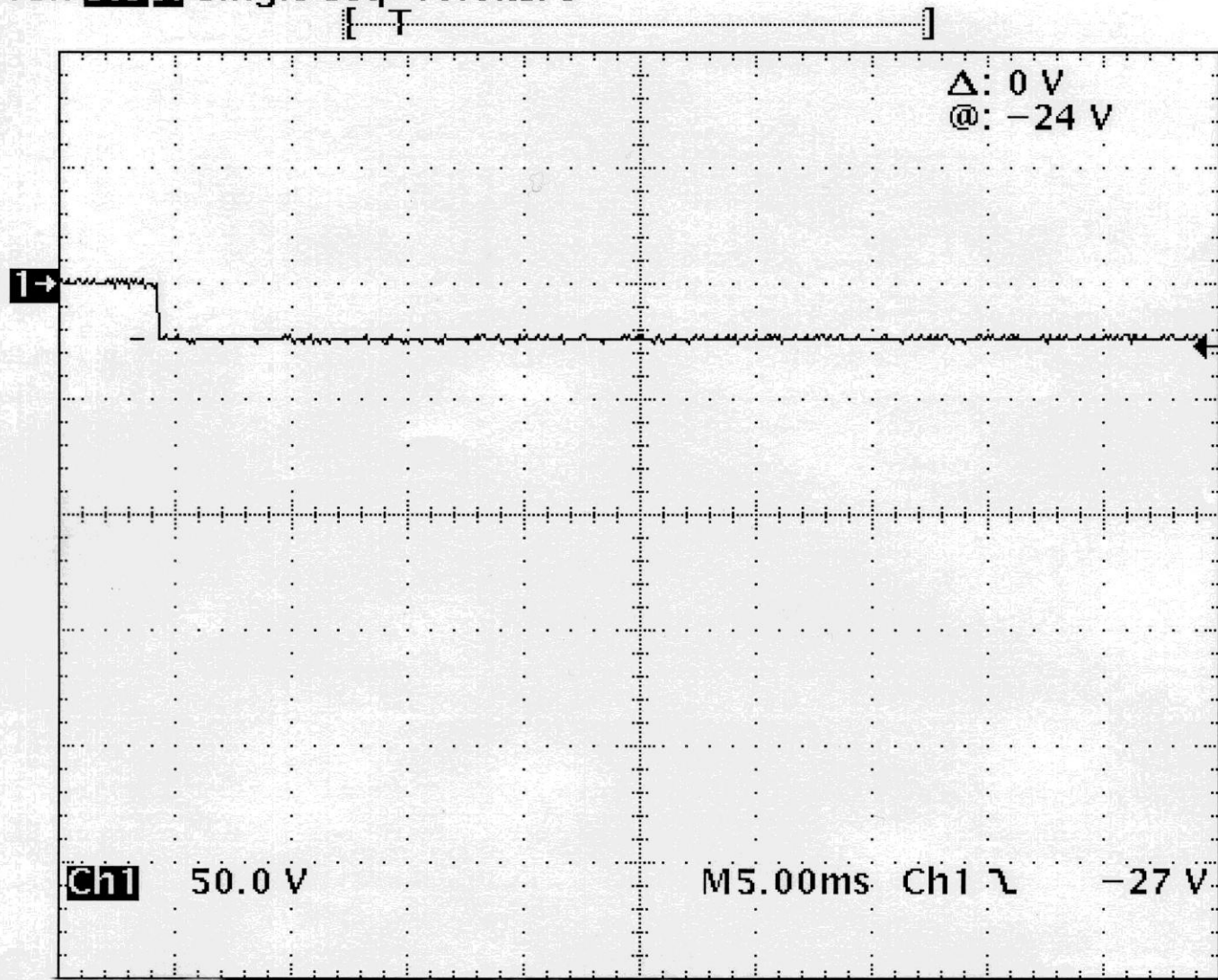


PLC-RSC-24DC/21 with inductive kickback diode

# PLC-RELAY

inside
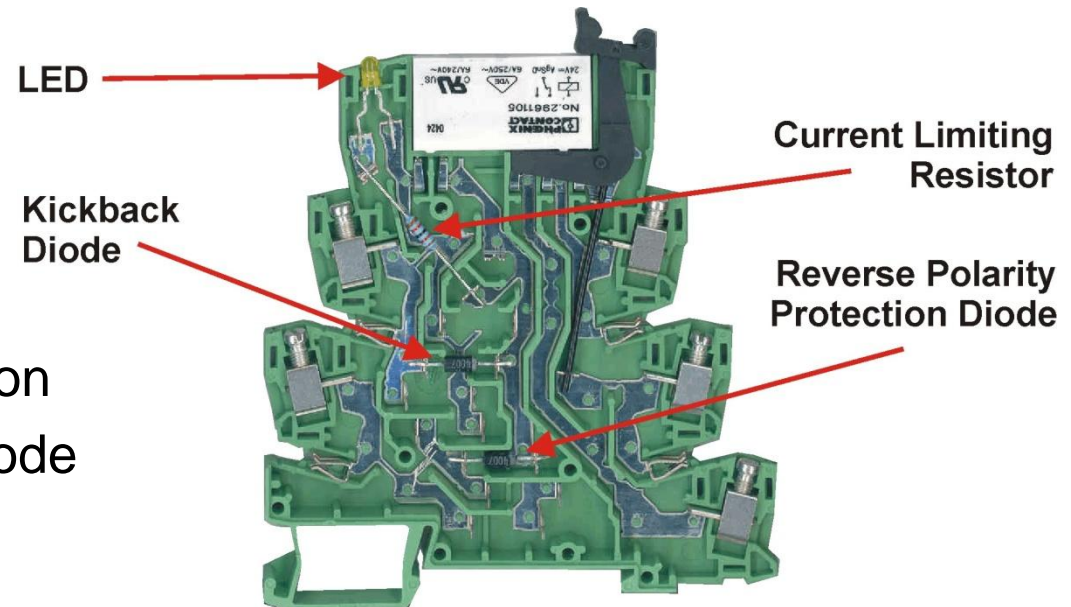
## ■ Base contains:

- LED
- Operation indication
- Reverse polarity diode
- Kickback diode
- Bridge rectifier



# Contact Load Types

What is the Application/Load?

- Resistive
- Capacitive
- Inductive
- Solid state

# Contact Load Types

- Incandescent lighting
- Electric heating elements
- Resistive loads generate heat



# Resistive Loads



# Contact Load Types

## Capacitive Loads

Capacitive = In-rush


- High current is demanded when voltage is first applied
- Types
  - Long transmission lines (wire distance adds capacitance)
  - Tungsten lamps (In-rush load, temperature sensitive)
  - Solenoids
  - Arc suppression
  - MOV's (Metal-Oxide Varistors) are capacitive
  - Power supplies
  - DC to DC converter (PLC)
  - AC motors (high inrush & inductive)
    - Especially with a capacitive start circuit



# Contact Load Types
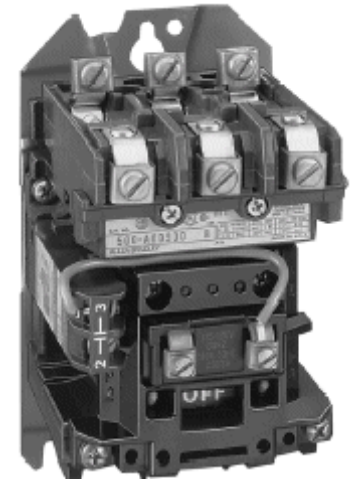
## Inductive Loads

- Motors (in-rush & inductive for AC)
  - Solenoids
  - Contactor Coils
  - **Relays**
  - Chokes & transformers
- 
- Inductors stores energy!
    - When the relay opens the circuit, the inductor will oppose the change in current (& collapse Magnetic Field)







# Contact Load Types


Small Signal

- PLC Input
- SSR

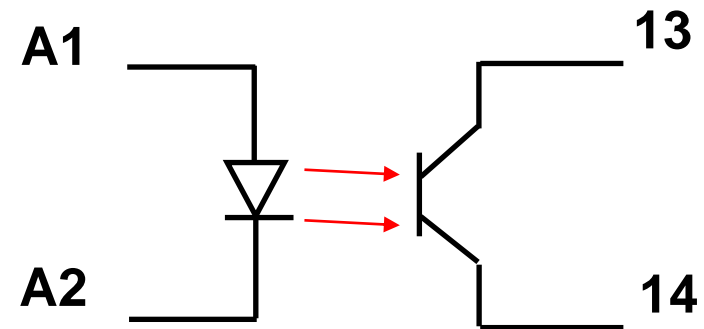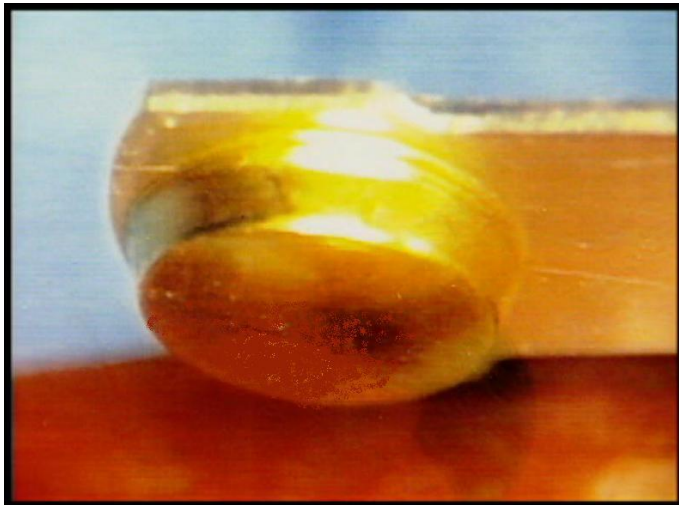

# Application Types


# Amplification

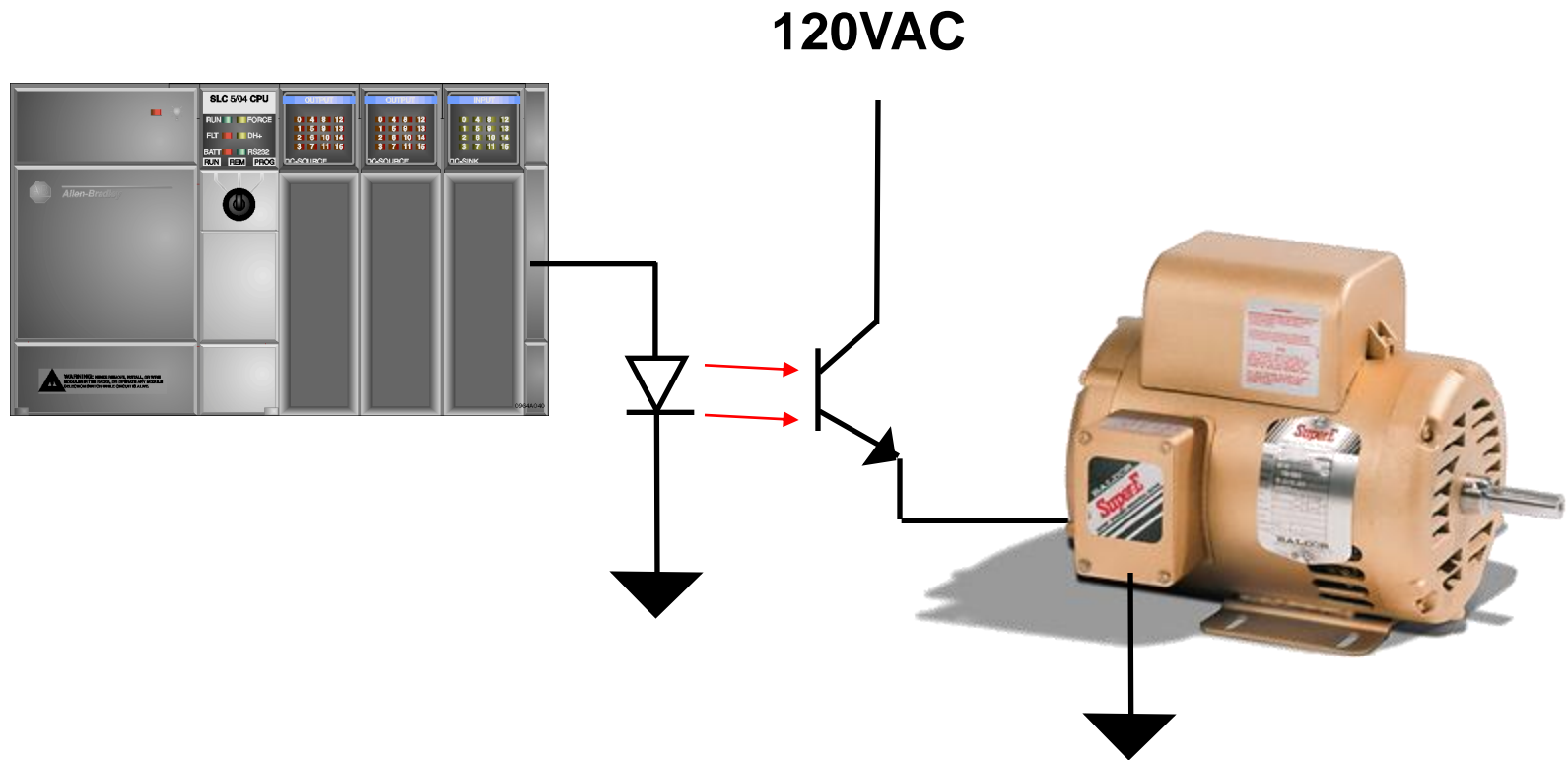

PLC with 24Vdc 500mA outputs.  
Application: Control 120Vac, 20A motor

# Application Types

# Voltage Conversion

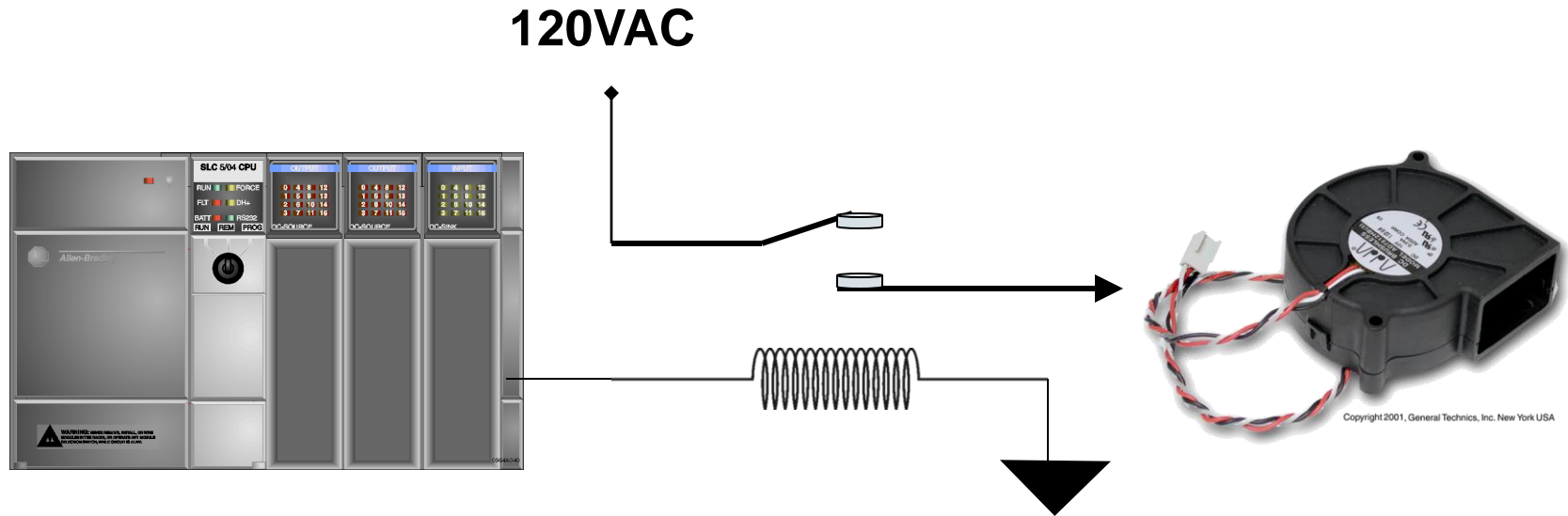


PLC with 24Vdc, 500mA outputs.

Application: Control 120Vac, 500ma blower

# Application Types

## Isolation

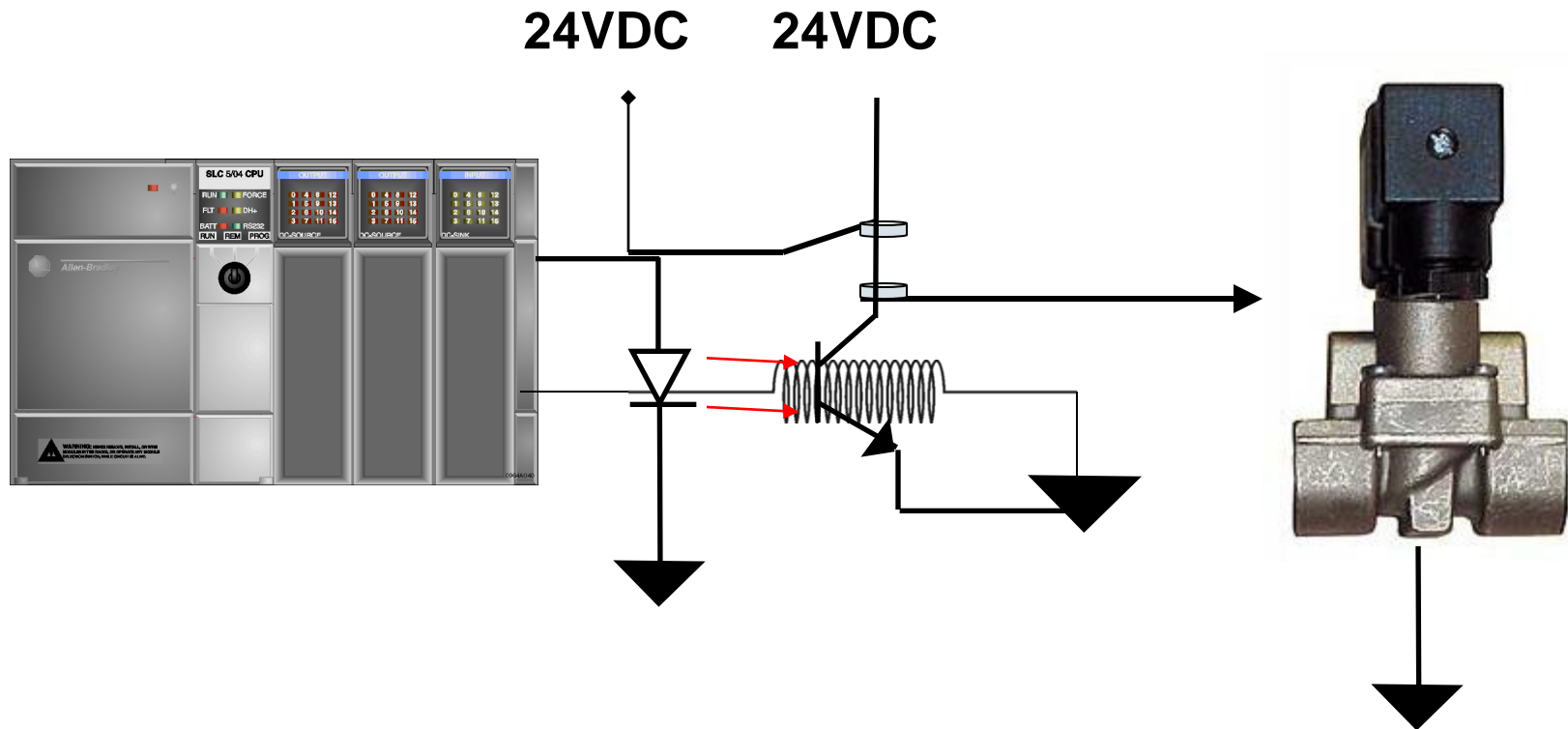

PLC with 24Vdc, 500mA outputs.

Application: Control 24Vdc, 500mA valve solenoid

**Thank You  
for  
your Attention**