

## Design Requirements

- Use Logisim to implement a set of instructions and the given circuit including a pipeline for Fetching, Decoding, and Executing our Instructions; Include the design of a Finite State Machine in our control unit logic to drive the pipeline.
- Design a piece of software to embed using our instruction set.
- Use an 8051 microcontroller simulator to perform the exact same task as our machine's embedded code; or some alternative assembly language execution (ARM, Motorola, etc.) Microcontroller or Microprocessor.
- Compare the performance of our machine to that of at least one existing assembly language.

### Op Codes

```

00h (OP-CODE = 00000000) Ri + counter#1 → Rk
01h (OP-CODE = 00000001) Ri + counter#2 → Rk
02h (OP-CODE = 00000010) Ri + Rj → Rk
03h (OP-CODE = 00000011) counter#1 + counter#2 → Rk
04h to 07h (OP-CODE = 000001XX) Reserved for subtraction instructions
08h (OP-CODE = 00001000) Ri x counter#1 → Rk, overflow → Rk+1
09h (OP-CODE = 00001001) Ri x counter#2 → Rk, overflow → Rk+1
0Ah (OP-CODE = 00001010) Ri x Rj → Rk, overflow → Rk+1
0Bh (OP-CODE = 00001011) counter#1 x counter#2 → Rk, overflow → Rk+1
0Ch to 0Fh (OP-CODE = 000011XX) Reserved for division instructions
10h (OP-CODE = 00010000) Compare Ri with counter#1 → Rk
11h (OP-CODE = 00010001) Compare Ri with counter#2 → Rk
12h (OP-CODE = 00010010) Compare Ri with Rj → Rk
13h (OP-CODE = 00010011) Compare Counters
14h (OP-CODE = 00010100) Ri AND counter#1 → Rk
15h (OP-CODE = 00010101) Ri AND counter#2 → Rk
16h (OP-CODE = 00010110) Ri AND Rj → Rk
17h (OP-CODE = 00010111) AND counters → Rk
18h (OP-CODE = 00011000) Ri OR counter#1 → Rk
19h (OP-CODE = 00011001) Ri OR counter#2 → Rk
1Ah (OP-CODE = 00011010) Ri OR Rj → Rk
1Bh (OP-CODE = 00011011) OR counters → Rk
1Ch to 1Fh (OP-CODE = 000111XX) Reserved for future instructions
20h to FFh Reserved for future instructions
    
```


### Simplified Functions

```

Ma1 = AC      Mb1 = ABC + E
Ma0 = ABC + DE  Mb0 = ABC + D'E'
Da2 = A'B + BC + AB'C'  Da1 = A'B' + B'C' + ABC
Da0 = AB' + B'C + A'BC'  Db2 = AB'C' + BC + A'B
Db1 = B'C' + ABC + A'B'  Db0 = AB' + ACE + A'BC' + B'C
    
```

### Truth Table for Control Logic



	A	B	C	D	E	Ma1	Ma0	Mb1	Mb0	Da2	Da1	Da0	Db2	Db1	Db0
ADD	0	0	0	0	0	0	0	0	1	0	1	0	0	1	0
	1	0	0	0	0	1	0	0	1	0	0	1	0	0	1
	2	0	0	0	1	0	0	0	0	0	1	0	0	1	0
	3	0	0	0	1	1	0	1	1	0	1	0	0	1	0
SUB	4	0	0	1	0	0	0	0	0	1	0	1	0	1	1
	5	0	0	1	0	1	0	0	1	0	0	1	1	0	1
	6	0	0	1	1	0	0	0	0	0	1	1	0	1	1
	7	0	0	1	1	1	0	1	1	0	0	1	1	0	1
MULT	8	0	1	0	0	0	0	0	1	1	0	1	1	0	1
	9	0	1	0	0	1	0	0	1	0	1	0	1	1	0
	10	0	1	0	1	0	0	0	0	1	0	1	1	0	1
	11	0	1	0	1	1	0	1	1	0	1	0	1	1	0
DIV	12	0	1	1	0	0	0	0	0	1	1	0	0	1	0
	13	0	1	1	0	1	0	0	1	0	1	0	0	1	0
	14	0	1	1	1	0	0	0	0	1	0	0	1	0	0
	15	0	1	1	1	1	0	1	1	0	1	0	0	1	0
COMP	16	1	0	0	0	0	0	0	0	1	1	1	1	1	1
	17	1	0	0	0	1	0	0	1	0	1	1	1	1	1
	18	1	0	0	1	0	0	0	0	1	1	1	1	1	1
	19	1	0	0	1	1	0	1	1	0	1	1	1	1	1
AND	20	1	0	1	0	0	0	0	1	0	0	1	0	0	1
	21	1	0	1	0	1	0	0	1	0	0	1	0	0	1
	22	1	0	1	1	0	0	0	0	0	0	1	0	0	1
	23	1	0	1	1	1	0	1	1	0	0	0	1	0	0
OR	24	1	1	0	0	0	0	0	1	0	0	0	0	0	0
	25	1	1	0	0	1	0	0	1	0	0	0	0	0	0
	26	1	1	0	1	0	0	0	0	0	0	0	0	0	0
	27	1	1	0	1	1	0	1	1	0	0	0	0	0	0
STORE	28	1	1	1	0	0	1	1	1	1	1	1	1	1	1
ROM	29	1	1	1	0	1	1	1	1	1	1	1	1	1	1
X	30	1	1	1	1	0	X	X	X	X	X	X	X	X	X
X	31	1	1	1	1	1	X	X	X	X	X	X	X	X	X

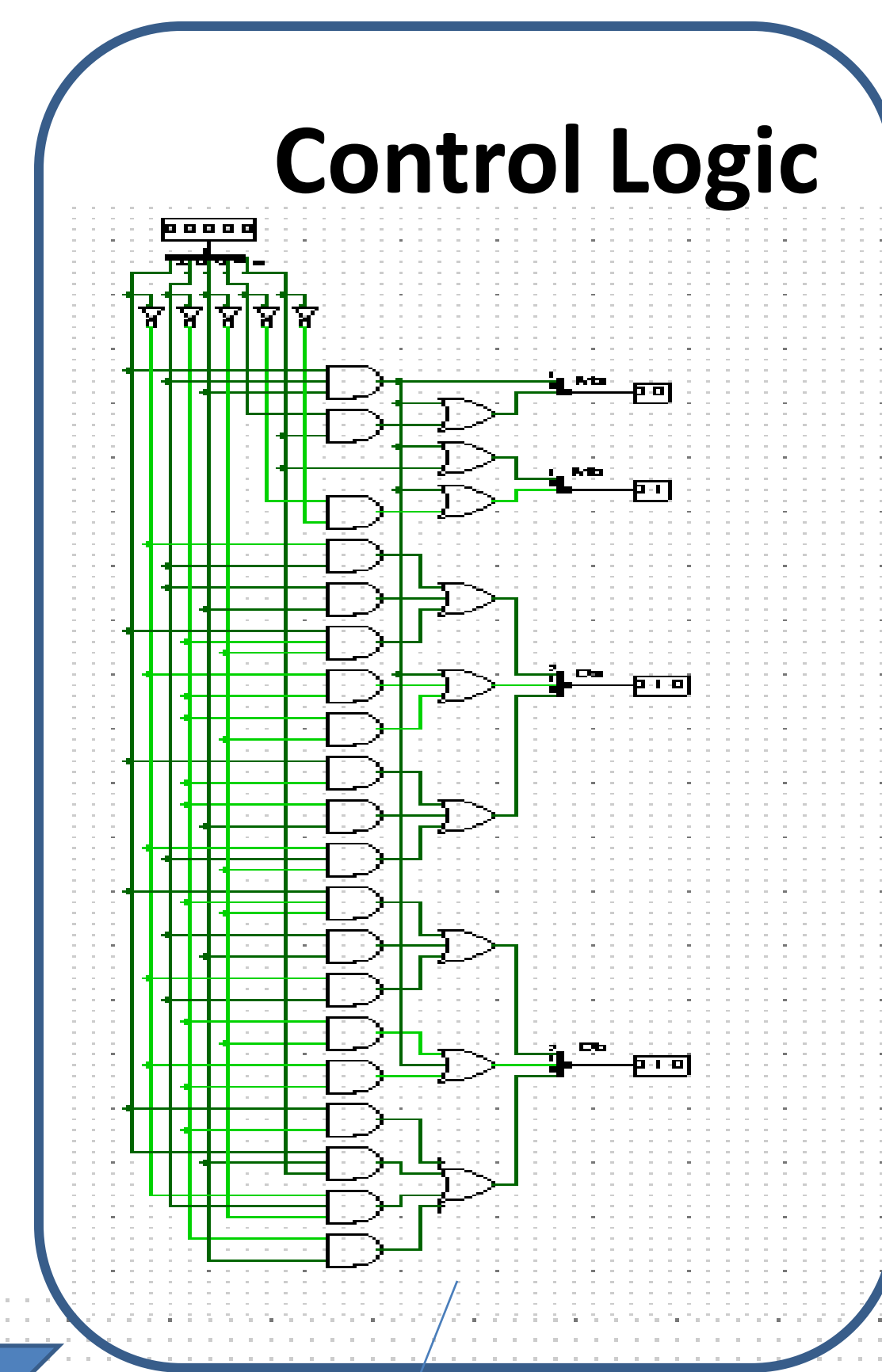

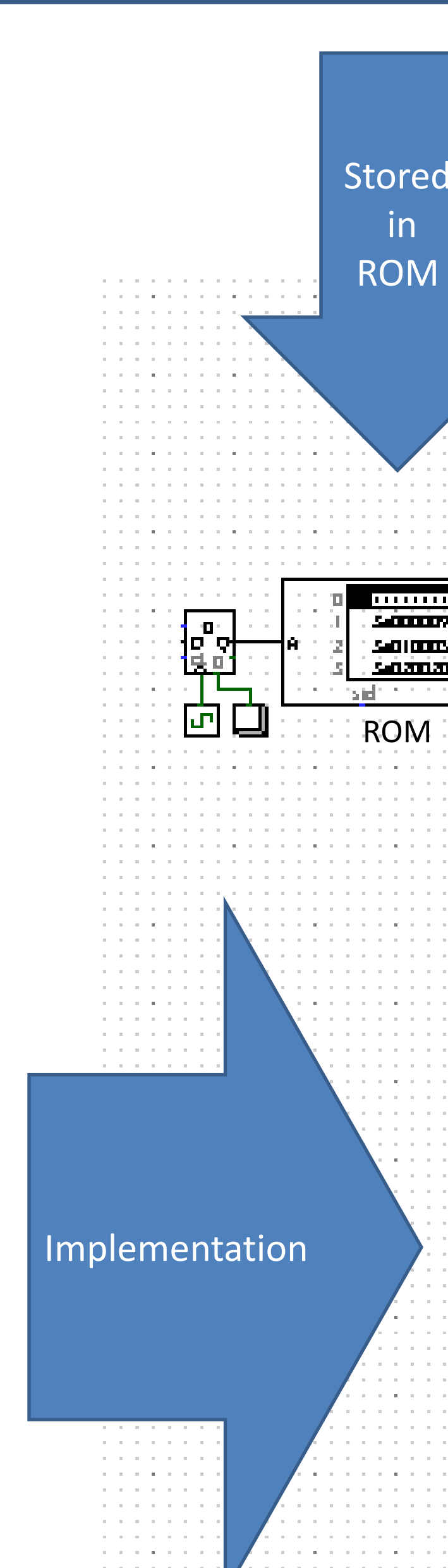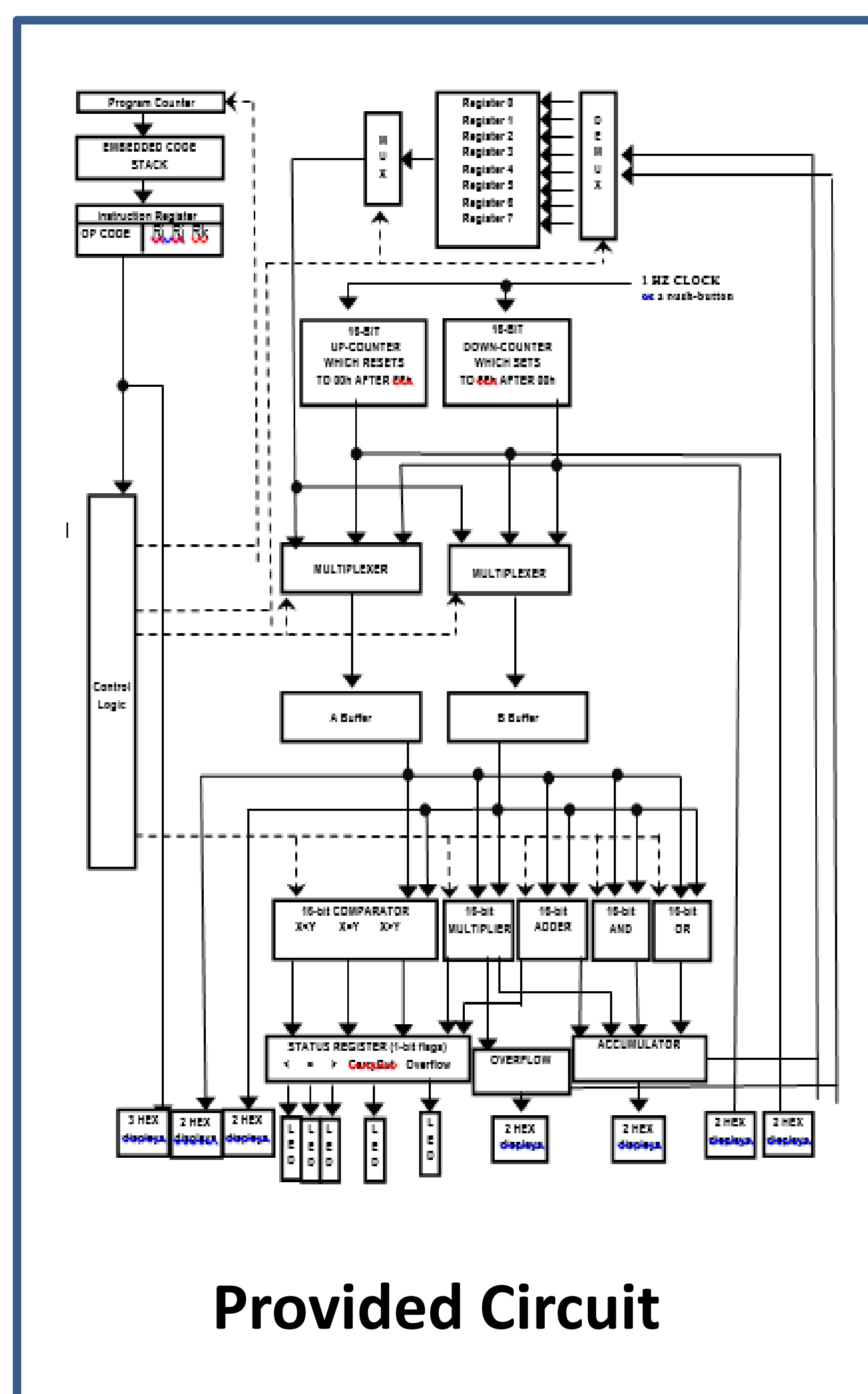
### Intel Assembly Code for Celsius to Fahrenheit

```

.file "convert.c"
.section .rodata
.LC0:
.string "%d"
.LC1:
.string "%d\n"
.text
.globl main
.type main, @function
main:
.LFB0:
.cfi_startproc
pushq %rbp
.cfi_def_cfa_offset 16
.cfi_offset 6, -16
movq %rsp, %rbp
.cfi_def_cfa_register 6
subq $16, %rsp
movl $.LC0, %eax
leaq -8(%rbp), %rdx
movq %rdx, %rsi
movq %rax, %rdi
movl $0, %eax
call __isoc99_scanf
movl -8(%rbp), %edx
movl %edx, %eax
sall $3, %eax
leal (%rax,%rdx), %ecx
movl $1717986919, %edx
movl %ecx, %eax
imull %edx
sarl %edx
movl %ecx, %eax
sarl $31, %eax
movl %edx, %ecx
subl %eax, %ecx
movl %ecx, %eax
addl $32, %eax
movl %eax, -4(%rbp)
movl $.LC1, %eax
movl -4(%rbp), %edx
movl %edx, %rsi
movq %rax, %rdi
movl $0, %eax
call printf
movl $0, %eax
leave
.cfi_def_cfa 7, 8
ret
.cfi_endproc
.LFE0:
.size main, .-main
.ident "GCC: (Ubuntu/Linaro 4.6.3-1ubuntu5) 4.6.3"
.section .note.gnu-stack,"",@progbits
    
```




### Complete Circuit

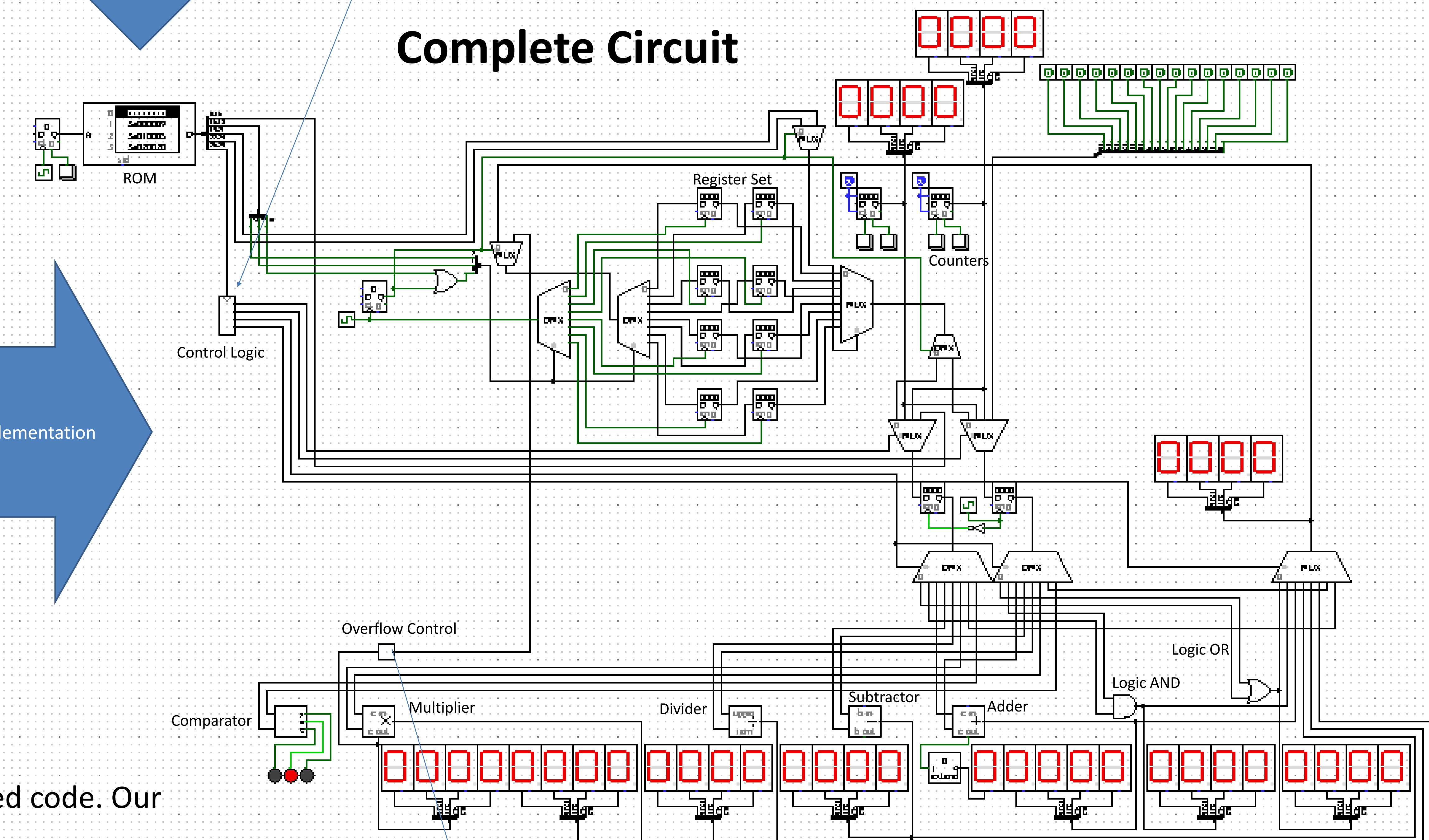

We used the Intel x86 Assembly language to perform the task as our machine's embedded code. Our program can successfully convert a Celsius value to Fahrenheit. Below are the opcodes of our program converted into hexadecimal for Logisim.
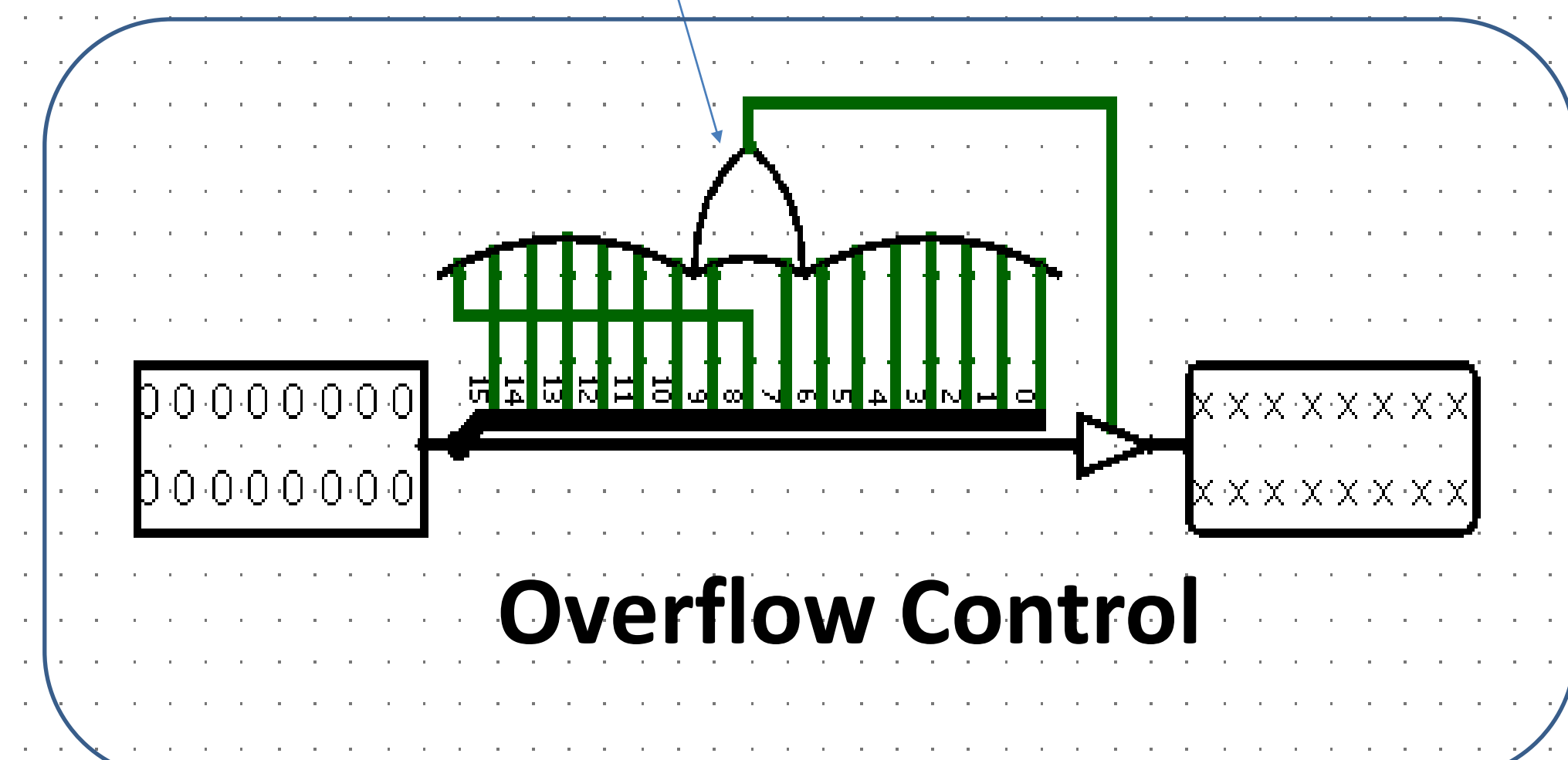
### ROM embedded Code for Celsius to Fahrenheit

00000000 3a000009 3a010005 3a020020  
 38030000 14c40000 1c650000 05540000  
 00000000



# Computer Design Competition

Tucker Strausbaugh  
 Sajid Amir  
 Kyler Killinger

EGR 433: Advanced Computer Engineering  
 Elizabethtown College, Elizabethtown, PA

